


Homework 2

ENEE 359a: Digital VLSI Design, Spring 2007

Assigned: Tue, Feb 20 Due: Tue, Feb 27

 1. Logic to Circuit to Layout


Convert the following logical expressions to schematic diagrams for static CMOS logic. Then convert each to a rough layout assuming an n-well process (e.g. p-type wafer: nFETs can be built directly on the wafer); you need only show wells for pFETs. The following is an example:




- A. $out = \sim((a \cdot b) | c)$
- B. $out = \sim((a | b) \cdot c)$
- C. $out = \sim(a \cdot b \cdot (c | d))$
- D. $out = (a + b)$; $c_{out} = (a + b = 10_2)$ (carry-out only; no carry-in)
 [do the full circuit diagram, but do not spend more than 20 minutes trying to do the layout for this; it is not simple AOI logic ... make enough of an attempt to understand the difficulty of dealing with inverted values]

2. Layout to Circuit to Logic


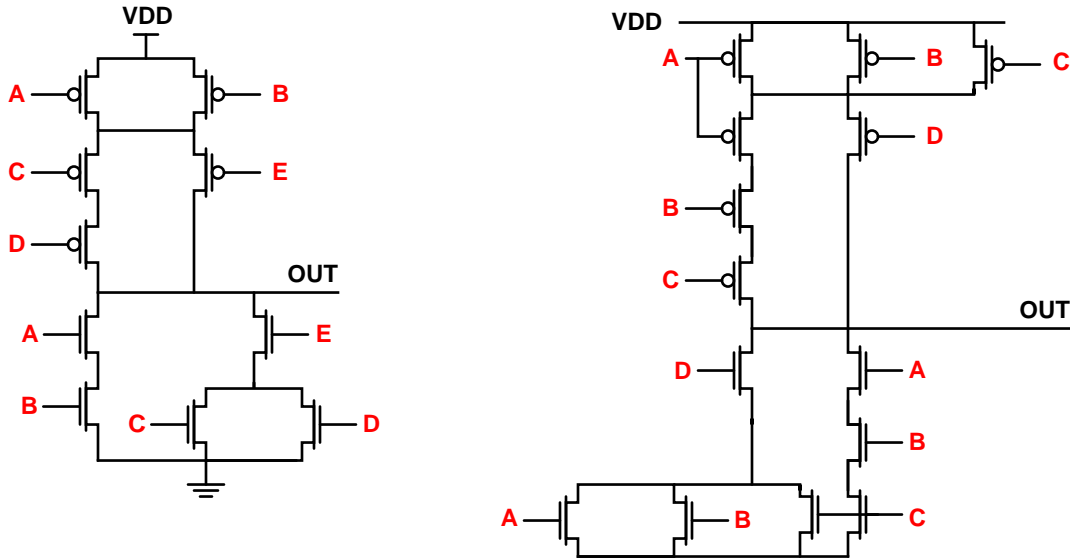
A. What logic equations do the following schematics implement?



 B. Consider the following stick diagram. Draw the transistor-level schematic. What logic equation does the circuit implement?



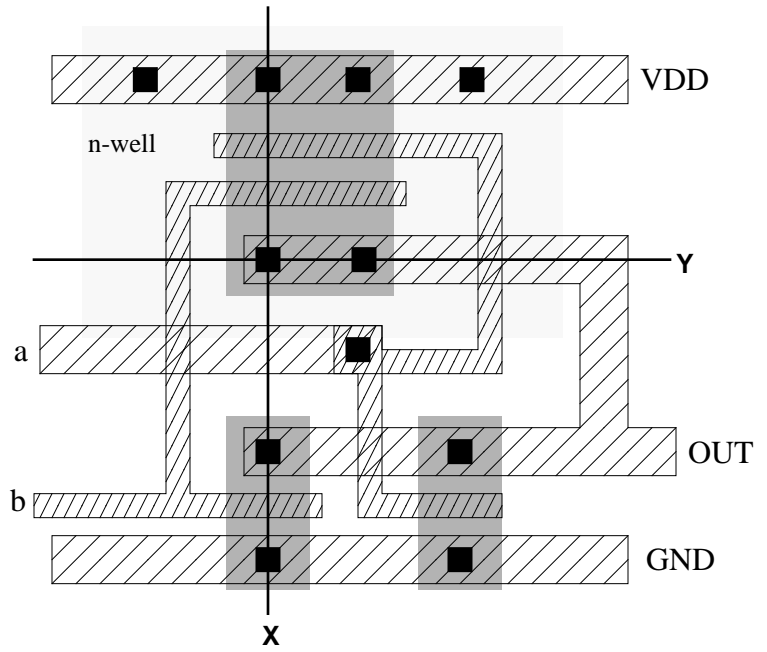 C. Provide a side-view diagram for each of the cuts X and Y through the layout below. Be sure to label each of the strata.



D. What is the logic equation represented by the layout in question C?