

Solutions

ECE Written Qualifying Examination, Summer 2017 Digital Logic

1. (4 points) Boolean Simplification.

Give an example of a pair of Boolean functions $f(x, y, z), g(x, y, z)$ such that $f(x, y, z)$ has more minterms than $g(x, y, z)$ but the cost of the minimal sum-of-products for f is less than the cost of the minimal sum-of-products for g .

		yz			
		00	01	11	10
0	1	1	0	0	
1	1	1	0	0	

f

		yz			
		00	01	11	10
0	1	0	0	0	
1	0	0	0	0	

g

$$f(x, y, z) = \bar{y}$$

$$g(x, y, z) = \bar{x}\bar{y}\bar{z}$$

2. (4 points) Boolean Algebra.

Using Boolean Algebra postulates and theorems prove that

$$\bar{x}\bar{y} + xz = (\bar{x} + z)(x + \bar{y})$$

No credit will be given for solutions that use the truth table method.

$$RHS = (\bar{x} + z)(x + \bar{y})$$

$$= \bar{x} \cdot x + \bar{x}\bar{y} + zx + z\bar{y}$$

(distributive)

$$= 0 + \bar{x}\bar{y} + zx + z\bar{y}$$

(complement)

$$= \bar{x}\bar{y} + zx + z\bar{y}$$

(additive identity)

$$= \bar{x}\bar{y} + zx + z\bar{y} \cdot 1$$

(multiplicative identity)

$$= \bar{x}\bar{y} + zx + z\bar{y}(x + \bar{x})$$

(complement)

$$= \bar{x}\bar{y} + zx + z\bar{y}x + z\bar{y}\bar{x}$$

(distributive)

$$= (\bar{x}\bar{y} + z\bar{x}\bar{y}) + (zx + zx\bar{y})$$

(commutative, associative)


$$= \bar{x}\bar{y} + zx = LHS$$

(absorption)

3. (7 points) Synthesis.


Design a 4-input, 1-output minimal two-level gate combinational network that gets as input a 4-bit number ($x = x_3x_2x_1x_0$) and outputs 0 if $0 \leq x \leq 4$ or $8 \leq x \leq 12$ and outputs 1 otherwise. [Note this circuit will detect the presence of any of the six illegal code groups in the 5421 code by providing a 1 output.]

x_3	x_2	x_1	x_0	f Out
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

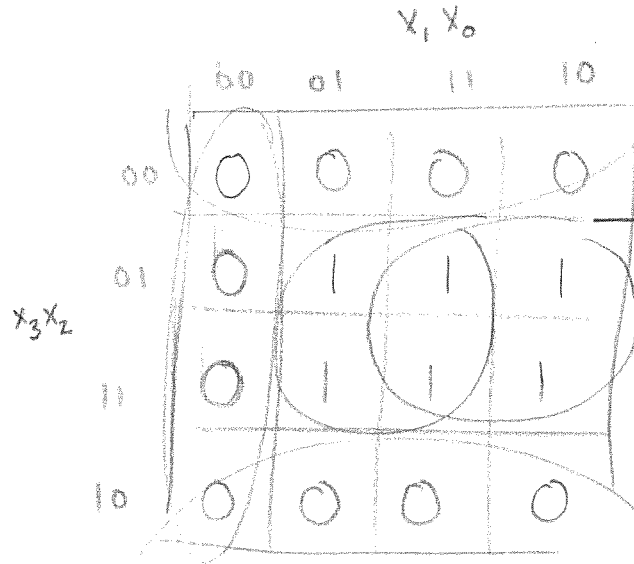

$$f = x_2 x_0 + x_2 x_1$$
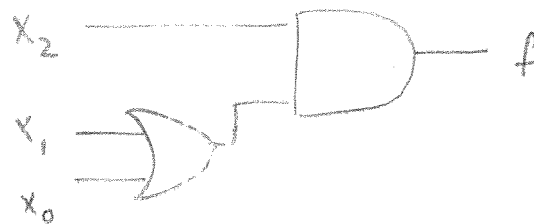
$$f = x_2 \cdot (x_1 + x_0) \quad \checkmark \text{ minimal}$$



4. (5 points) State Diagram.

Draw the state diagram of a Mealy machine having a single input line x , in which the symbols 0 and 1 are applied, and a single output line z . For $i = 1, 2, 3, \dots$ let x_i denote the i -th input symbol. For $i \geq 3$, the system is to produce an output of 1 coincident with input symbol x_i if the previous 3 bits (from right to left) $(x_i, x_{i-1}, x_{i-2}, x_{i-3})$ form a palindrome (i.e. $(x_i, x_{i-1}, x_{i-2}, x_{i-3}) = (x_{i-3}, x_{i-2}, x_{i-1}, x_i)$). At all other times the system is to output 0. An example of input/output sequences that satisfy the conditions of the system specification is:

$x = 0 \ 1 \ 0 \ 0 \ 1 \ 0 \ 0 \ 1 \ 1 \ 0 \ 1$
 $z = 1 \ 0 \ 0 \ 1 \ 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 0$

In the example above, the system produces an output of 1 coincident with the 3-rd input symbol. This occurs since the 1-st, 2-nd and 3-rd input symbols are 1, 0, 1, which is a palindrome.

