
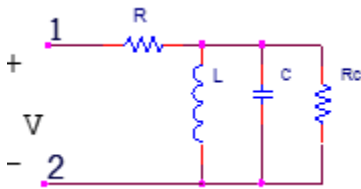


#1. (7 points)

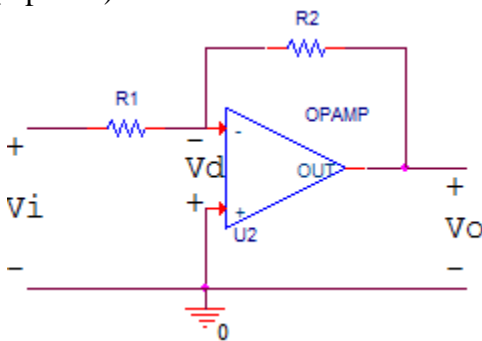

- For the above circuit find the input admittance,  $y_{in}(s)$ , seen between nodes 1 and 2. Present the results as a polynomial numerator over polynomial denominator.
- Give the conditions for this circuit to become a sinusoidal oscillator when there is a short circuit between nodes 1 and 2.

#. (6 points)



In the above circuit the op-amp has no current into its + & - leads and has the open circuit complex frequency gain (for which  $K$  and  $\sigma$  are positive numbers)

$$\frac{V_o}{V_d}(s) = \frac{K}{s+\sigma}$$

- Give the circuit gain

$$\frac{V_o}{V_i}(s)$$


- What type of filter is this?

#3. (7 points)

For the following diode circuit assume the diode,  $D_v$ , is described by the voltage  $V$  controlled by the current  $I$  via the cubic law:

$$V = V_d + K_d[I^3 - 10^{-6}I] \quad V_d = 1V, K_d = 6 \times 10^8 \text{ V/A}^3$$

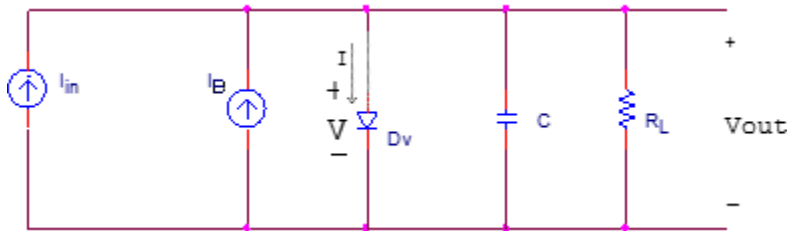In the circuit  $C = 20\text{nFd}$ .  $I_B = 2\text{mA}$  is a bias current and  $I_{in}$  is a small signal current.



- Sketch the diode  $V$  vs.  $I$  curve for  $-2\text{mA} < I < +2\text{mA}$  giving the local maxima and minima values of  $V$ .
- Add a load line passing through the point  $V=0$  at  $I=I_B$ , the bias current point of  $I_B = 2\text{mA}$ , as well as the Q point,  $V=V_Q$  at  $I=I_Q=0$ .
- Find the value of the load resistance,  $R_L$ , to give this load line.
- Find the small signal diode resistance  $r_d$  at the Q point.
- Give the small signal differential equation for  $V_{out}(t)$  with  $I_{in}(t)$  as forcing function.
- Give the small signal transfer function.  $T(s) = \frac{V_{out}}{I_{in}}(s)$


Solutions - Circuits S2017

#1. a) 
$$y_{in} = \frac{1}{R + \frac{1}{CA + G_C + \frac{1}{LA}}} = \frac{1}{R + \frac{LA}{LCa^2 + LG_C a + 1}} = \frac{LCa^2 + LG_C a + 1}{RLCa^2 + RL G_C a + LA}$$

$(G_C = 1/R_C)$

$= \frac{LCa^2 + \frac{L}{R_C} a + 1}{RLCa^2 + (\frac{RL}{R_C} + L)a + R} = \frac{1}{R} \left[ \frac{a^2 + \frac{1}{R_C} a + \frac{1}{LC}}{a^2 + \frac{1}{R} (\frac{RL}{R_C} + L)a + \frac{1}{LC}} \right]$


b)  $I = y_{in}(s)V$   
 If node 1 is shorted to node 2,  $V=0 \Rightarrow I \neq 0$  if  $y_{in}(s) \rightarrow \infty$   
 $D(s) = RLCs^2 + L(\frac{R}{R_C} + 1)s + 1 = 0$ ; For non-oscillatory  $D(s) = as^2 + b$   
 $\Rightarrow RLC(a^2 + \frac{1}{RLC}) = 0$  with  $\frac{1}{RLC} > 0 \Rightarrow \frac{R}{R_C} = -1 \Rightarrow \underline{\underline{R_C = -R < 0}}$


#2. a)  
$$\begin{aligned} v_d &= R_1 i - v_0 \Rightarrow i = G_1(v_d + v_0), G_1 = 1/R_1 \\ -v_d &= R_2 i + v_0 \Rightarrow -v_d = R_2 G_1(v_d + v_0) + v_0 \\ \Rightarrow -(1 + R_2 G_1)v_d &= R_2 G_1 v_0 + v_0 \\ \Rightarrow -(1 + R_2 G_1) \frac{(a + s_0)}{K} v_0 &= R_2 G_1 v_d + v_0 \Rightarrow \left[ -\frac{(1 + R_2 G_1)(a + s_0)}{K} - 1 \right] v_0 = R_2 G_1 v_d \\ \Rightarrow \frac{v_0}{v_d}(s) &= \frac{-R_2 G_1 K}{[(1 + R_2 G_1)(a + s_0) + K]} = \frac{-[R_2 G_1 K] / (1 + R_2 G_1)}{a + (s_0 + \frac{K}{1 + R_2 G_1})} \end{aligned}$$

b) This is a low pass filter as  $\frac{v_0}{v_d} \rightarrow 0$  monotonically as  $a \rightarrow \infty$

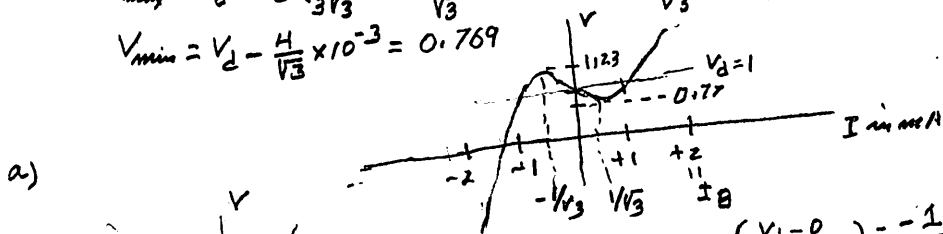
#3. @  $I = \pm 10^{-3}$ ,  $V \approx V_d = 1$ , @  $I = -2 \times 10^{-3}$ ,  $V = 1 - 6 \times 10^8 (8 \times 10^{-9} - 2 \times 10^{-9}) = 1 - 3.6 = -2.6$   
 @  $I = +2 \times 10^{-3}$ ,  $V = 1 + 6 \times 10^8 (8 \times 10^{-9} - 2 \times 10^{-9}) = 1 + 3.6 = 4.6$

Max/Min  $\Rightarrow dV/dI = K_d(3I^2 - 10^{-6}) = 0 \Rightarrow I = \pm \frac{1}{\sqrt{3}} \text{ mA} \Rightarrow$   
 $V_{max} = V_d - K_d \left( \frac{1}{3\sqrt{3}} \times 10^{-9} - \frac{1}{\sqrt{3}} \times 10^{-9} \right) = 1 + \frac{6 \times 10^8}{\sqrt{3}} \left( 1 - \frac{1}{3} \right) = 1 + \frac{4}{\sqrt{3}} \times 10^8 = 2.231$   
 $V_{min} = V_d - \frac{4}{\sqrt{3}} \times 10^8 = 0.769$



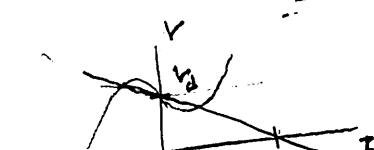a)   
 b)  $R_L = -\text{slope} = -\left( \frac{V_d - 0}{0 - I_B} \right) = \frac{-1}{-2 \times 10^{-3}} = \frac{1000}{2} = 500 \Omega$

c)  $d) v_d = \frac{dV}{dI} = K_d(3I^2 - 10^{-6}) \Big|_{I=0} = -K_d \times 10^{-6} = -6 \times 10^8 \times 10^{-6} = -600 \Omega$

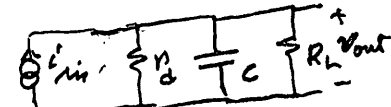e)  
$$i_{in} = [(g_d + G_L) + sC] v_{out} \Rightarrow C \frac{dv_{out}}{dt} + (g_d + G_L) v_{out} = i_{in}$$
  
 $g_d = 1/R_d = -1/600, G_L = 1/500$

f) 
$$\frac{v_{out}}{i_{in}}(s) = \frac{1}{Cs + (g_d + G_L)} = \frac{1}{20 \times 10^{-9} s + 0.33 \times 10^{-3}} = \frac{(1/2) \times 10^8}{s + 1.667 \times 10^4}$$