

Solutions

ECE Written Qualifying Examination, Winter 2017 Digital Logic

1. (4 points) Boolean Simplification.

Give an example of a pair of Boolean functions $(f_1(w, x, y, z), f_2(w, x, y, z))$ such that the minimal two-output network for f_1, f_2 contains a product term that is not a prime implicant of f_1 and not a prime implicant of f_2 . Justify your answer and draw the minimal two-output network.

	00	01	11	10	yz
00					
01		1	1	1	f_1
11		1			
10		1			
		f_2			


minimize $f_1: \bar{w}xz + \bar{w}xy$

minimize $f_2: x\bar{y}z + w\bar{y}z$

combined $f_1, f_2: \bar{w}x\bar{y}z + \bar{w}xy$
 $\bar{w}x\bar{y}z + w\bar{y}z$

cost:
 $\frac{8}{8} = 16$

$= 14$

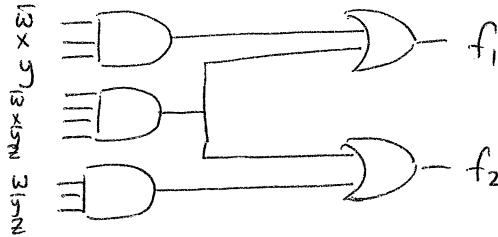

2. (4 points) Boolean Algebra.

Using Boolean Algebra postulates and theorems Prove that

$$\bar{x}z + x\bar{y} = \bar{y}z + \bar{x}z + x\bar{y}.$$

No credit will be given for solutions that use the truth table method.

Hint: Start by multiplying one of the product terms on the right hand side by 1.

$$\begin{aligned} \text{RHS} &= \bar{y}z + \bar{x}z + x\bar{y} \\ &= \bar{y}z \cdot 1 + \bar{x}z + x\bar{y} \\ &= \bar{y}z(x + \bar{x}) + \bar{x}z + x\bar{y} \\ &= \bar{y}z x + \bar{y}z \bar{x} + \bar{x}z + x\bar{y} \\ &= \bar{x}z + \bar{x}z \bar{y} + x\bar{y} + x\bar{y}z \\ &= \bar{x}z + x\bar{y} \\ &= \text{LHS} \end{aligned}$$

multiplicative identity
 complement
 distributive
 commutative
 absorption

3. (6 points) The following figure gives the circuit diagram of a mod-10 counter that counts the sequence 0000, 0001, 0010, ..., 1001, and then repeats from 0000.



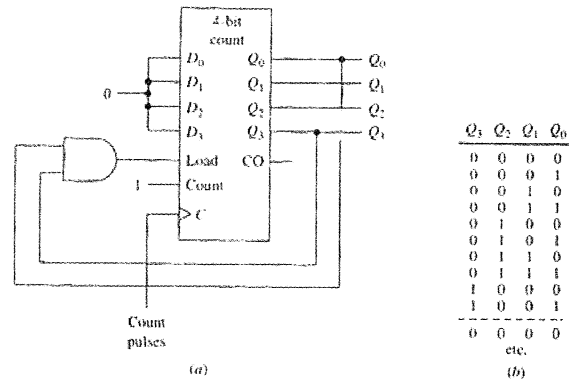


Figure 6.35 Synchronous mod-10 counter. (a) Connections (b) Counting sequence.

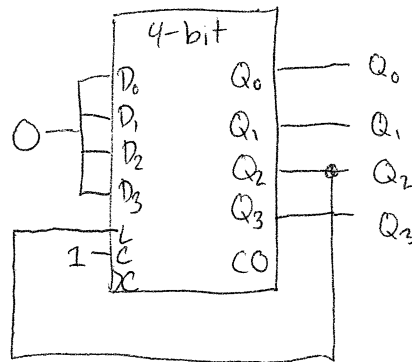- (a) (3 points) Draw a similar circuit diagram for a mod-5 counter that counts the sequence 0000, 0001, 0010, 0011, 0100, and then repeats from 0000.



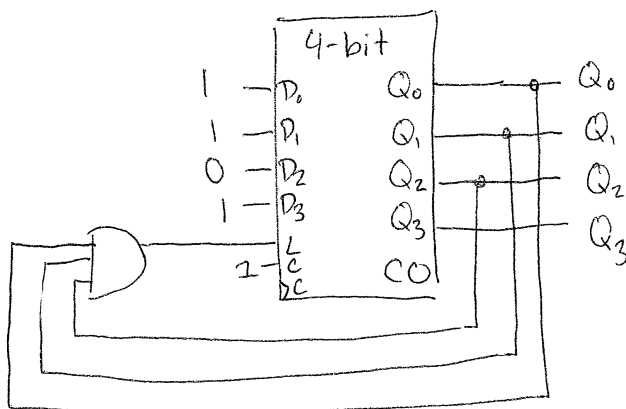- (b) (3 points) Draw a similar circuit diagram for a mod-5 counter that counts the sequence 1011, 1100, 1101, 1110, 1111, and then repeats from 1011.



4. (6 points) State Diagram. You are given the state diagrams of two single-input, single-output Mealy-model finite state machines (FSMs) A and B , both of which take the same input x . FSMs A and B have n_A and n_B number of states, respectively. Explain how you will use the state diagrams of A and B to draw the state diagram of a Mealy-model FSM C that takes x as input and outputs a 1 whenever A or B would output a 1 (and outputs a 0 otherwise). How many states will C have? How will you determine the transitions in C , given the transitions in A and B ?

Let S_A be the states of A

S_B be the states of B

Set of states of C : $S_C := \{(s_i, s_j) : s_i \in S_A, s_j \in S_B\}$

number of states: $n_A \cdot n_B$

initial state of C is (s_{Ainit}, s_{Binit}) where s_{Ainit}, s_{Binit} are initial states of A, B

for any pair of states $(s_i, s_j), (s_k, s_l) \in S_C$

there is an edge labeled $1/0$ ($0/0$) from (s_i, s_j) to (s_k, s_l)

iff: - There is an edge labeled $1/0$ ($0/0$) from s_i to s_k in A AND

- There is an edge labeled $1/0$ ($0/0$) from s_j to s_l in B

there is an edge labeled $1/1$ ($0/1$) from (s_i, s_j) to (s_k, s_l)

iff: - There is no $1/0$ ($0/0$) edge as above AND

- There is an edge labeled $1/*$ ($0/*$) from s_i to s_k in A

- There is an edge labeled $1/*$ ($0/*$) from s_j to s_l in B . AND