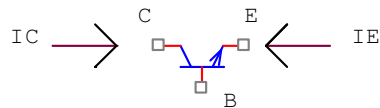



Circuits Fall 2018

- For the following circuits, unless otherwise stated, assume that the op-amp is ideal (zero input currents and zero input difference voltage [due to infinite gain]).
- And assume that a npn transistor is described by the Ebers-Moll model which has for the collector current:

$$I_C = \alpha I_{Eo} (1 - \exp(V_{BE}/V_T)) - I_{Co}(1 - \exp(V_{BC}/V_T))$$



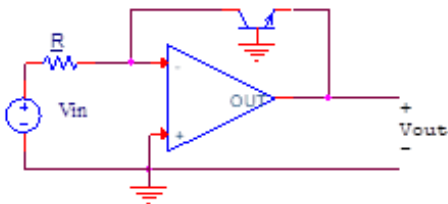
#1. (6 points) For the following feedback circuit:



- (4 points) Find  $V_{out}$  as a function of  $V_{in}$ .
- (2 points) If the op-amp is not ideal and actually saturates at supply bias voltages  $\pm V_{supply}$ , discuss limitations on the validity of your answer in part a)

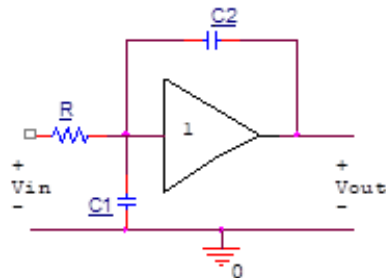
#2. (7 points) In the following circuit the amplifier is a unity voltage gain one with no input current



- (3 points) Find the transfer function  $V_{out}(s)/V_{in}(s)$
- (2 points) Give the zeros and poles of the transfer function and the unit impulse response.
- (2 points) Give an ideal op-amp realization of the amplifier.
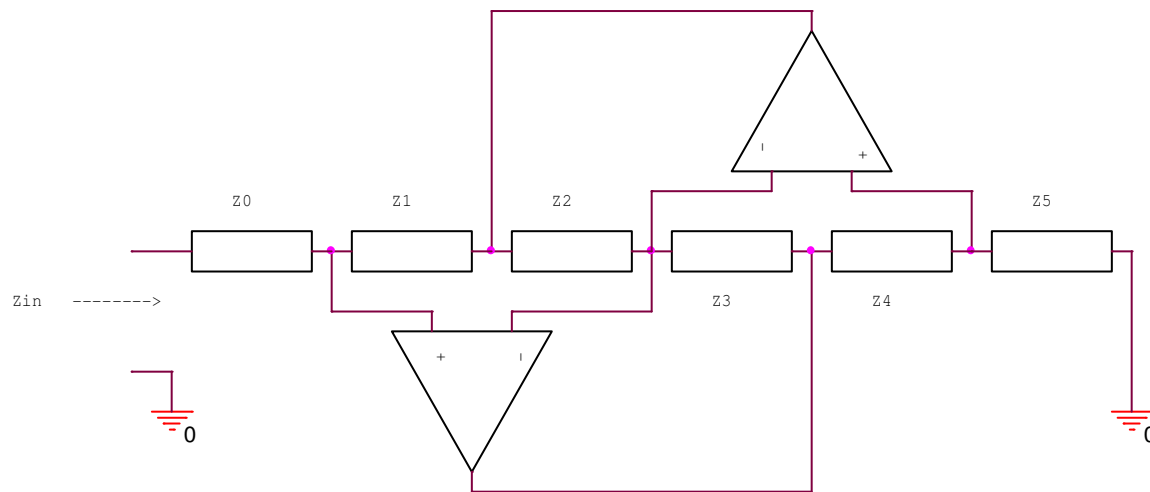
#3) (7 points) The following is a circuit diagram for a General Impedance Converter (GIC) for which the input impedance is given as:

$$Z_{in}(s) = Z_0(s) + \frac{Z_1(s) \cdot Z_3(s) \cdot Z_5(s)}{Z_2(s) \cdot Z_4(s)}$$



Choose Z2 and Z4 as equal capacitors of capacitance C and all other branches as resistors with equal resistance R.

- (2 points) Give  $Z_{in}(s)$  in terms of the chosen components.
- (3 points) Give the poles and zeros of  $Z_{in}(s)$ .
- (2 points) The circuit can be an oscillator. Give conditions for this and the oscillation frequency in terms of R and C.


Circuits F1018 solutions

#1. a) at  $v_{BC} = v_{sp.amp.in} = 0$  then  $I_C = \alpha I_{E_0} (1 - e^{V_{BE}/V_T}) = \alpha I_{E_0} (1 - e^{-V_{out}/V_T})$  as  $V_{BE} = -V_{out}$   
 and as  $v_{in.amp.in} = 0 \Rightarrow I_R = I_C = \alpha I_{E_0} (1 - e^{-V_{out}/V_T})$   
 $I_R = V_{in}/R = I_C = \alpha I_{E_0} (1 - e^{-V_{out}/V_T})$   
 $\Rightarrow \frac{V_{in}}{\alpha I_{E_0} R} - 1 = -e^{-V_{out}/V_T} \Rightarrow V_T \ln(1 - \frac{V_{in}}{\alpha I_{E_0} R}) = -V_{out} \Rightarrow V_{out} = -V_T \ln(1 - \frac{V_{in}}{\alpha I_{E_0} R})$

b) as  $-12 < V_{out} < +12$  outside of saturation  $-V < -V_T \ln(1 - \frac{V_{in}}{\alpha I_{E_0} R}) < +V$ ,  $V = |V_{supply}|$ , limits  $V_{in}$  to cover  $V_{out}$  in the  $\ln(\cdot)$  region.

#2. a) as the amplifier output voltage equals its input voltage the voltage on  $C_2$  is zero & no current flows into  $C_2$ . Then  $RC_1$  acts as a voltage divider  $V_{in} = \frac{R}{R+1/RC} V_{out} = \frac{1}{RCR+1} V_{out} = V_{out}$  by unity gain amplifier

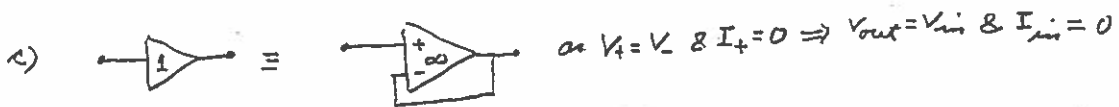b)  $T(s) = \frac{1}{RCR+1} = \frac{1/RC}{s + 1/RC} =$  transfer function  $\frac{V_{out}}{V_{in}}$ ; impulse response  $h(t) = \frac{1}{RC} e^{-t/RC} u(t)$   
 $\Rightarrow$  zero @  $s = \infty$ , pole @  $s + 1/RC = 0 \Rightarrow @ s = -1/RC$



#3. a)  $Z_2(s) = Z_4(s) = \frac{1}{Cs}$ ,  $Z_0 = Z_1 = Z_2 = Z_3 = R \Rightarrow Z_{in}(s) = R + R^2 \frac{1}{(\frac{1}{Cs})^2} = R + R^3 C^2 s^2$

b) poles, two @  $s = \infty$ , zeros  $\Rightarrow 0 = R + R^3 C^2 s^2 \Rightarrow s^2 = -\frac{R}{R^3 C^2} = -\frac{1}{(RC)^2} \Rightarrow \omega_0 = \pm j \frac{1}{RC}$

as  $V_{in}(s) = (R + R^3 C^2 s^2) I_{in}$

short circuit  $\Rightarrow V_{in} = 0 \Rightarrow I_{in} \neq 0$  if  $Z_{in}(s) = 0 \Rightarrow \omega_0$  are short circuit natural frequencies

open circuit  $\Rightarrow I_{in} = 0 \Rightarrow V_{in} \neq 0$  if  $Z_{in}(s) = \infty \Rightarrow s = \infty$  are open circuit natural frequencies

c) To be an oscillator initial conditions to excite the circuit to give sine waves. This occurs at the natural frequencies & for finite ones when the input is shorted and

$\omega_0 = j\omega_0 \Rightarrow \omega_0 = \frac{1}{RC} \equiv f_{osc} = \frac{1}{2\pi RC}$  Hertz