

Solutions

ECE Written Qualifying Examination, Fall 2018 Digital Logic

1. (5 points) Boolean Simplification.

Using the Quine-McCluskey method, obtain all the prime implicants for

$$f(x, y, z) = \sum m(0, 2, 3, 5, 7).$$

<u>(0) 000</u>	<u>(0,2) 0-0</u>
(2) 010	(2,3) 01-
<u>(3) 011</u>	(3,7) -11
(5) 101	(5,7) 1-1
<u>(7) 111</u>	

2. (5 points) Boolean Algebra.

Using Boolean Algebra postulates and theorems prove that


$$(x + z)(y + z)(\bar{y} + \bar{z}) = \bar{y}z + xy\bar{z}$$

No credit will be given for solutions that use the truth table method.

$LHS = (z+x)(z+y)(\bar{y} + \bar{z})$	Commutative
$= (z+xy)(\bar{y} + \bar{z})$	Distributive
$= z\bar{y} + xy\bar{y} + z\bar{z} + xy\bar{z}$	Distributive
$= \bar{y}z + x \cdot 0 + 0 + xy\bar{z}$	Complement
$= \bar{y}z + 0 + 0 + xy\bar{z}$	Null Elements
$= \bar{y}z + xy\bar{z} = RHS$	Identity

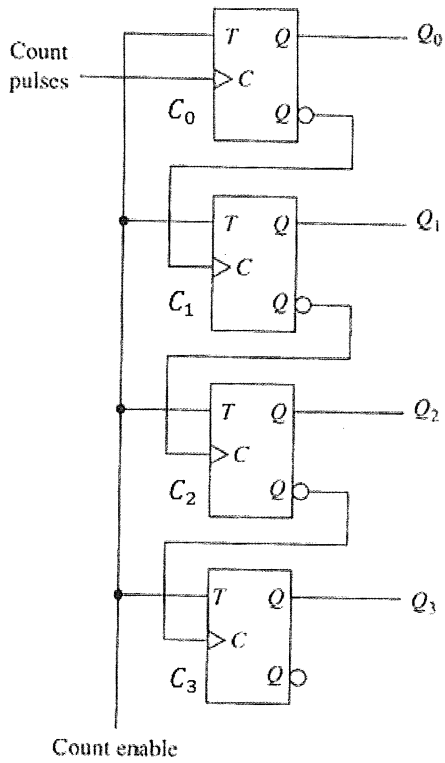3. (5 points) Counters.

For the binary ripple counter pictured below, fill in the following table which shows the values of $Q_0, Q_1, Q_2, Q_3, C_0, C_1, C_2, C_3$ during each clock pulse. Assume count enable is set to 1.



C_0	Q_0	C_1	Q_1	C_2	Q_2	C_3	Q_3
0	0	1	0	1	0	1	0
1	1	0	0	1	0	1	0
0	1	0	0	1	0	1	0
1	0	1	1	0	0	1	0
0	0	1	1	0	0	1	0
1	1	0	1	0	0	1	0
0	1	0	1	0	0	1	0
1	0	1	0	1	1	0	0
0	0	1	0	1	1	0	0
1	1	0	0	1	1	0	0

4. (5 points) State Diagram.

Draw the state diagram of a *minimal* Mealy machine having two input lines x, y , in which the signals $\{0, 1\}$ are applied, and a single output line z . For $i = 1, 2, 3, 4, \dots$ let x_i, y_i denote the i -th input values. For $i \geq 1$, the system is to produce an output of 1 coincident with input symbols x_i, y_i if the binary number represented by x_i, \dots, x_1 is greater than the binary number y_i, \dots, y_1 , where x_i and y_i are the most significant bits and x_1 and y_1 are the least significant bits. At all other times the system is to output 0.

An example of input/output sequences that satisfy the conditions of the system specification is:

i	1	2	3	4	5	6	7	8	9	10	11
x	1	0	1	1	1	0	1	0	1	1	0
y	1	1	1	0	0	1	1	0	0	1	0
z	0	0	0	1	1	0	0	0	1	1	1

In the example above, the system produces an output of 1 coincident with the 4-th input symbol. This occurs since the 1-st, 2-nd, 3-rd and 4-th input symbols are 1, 0, 1, 1 on the x input line and 1, 1, 1, 0 on the y input line, since $1101 > 0111$, the system outputs 1.

Your state diagram should have the minimum number of states possible.

