

ECE Written Qualifying Examination, Circuits Spring 2018

1. 7 points


The following NMOS circuit is biased for drain current $I_D=1\text{mA}$ using the battery of voltage $V_{DD}=9\text{V}$. Assume the transistor is described by

$$I_D=k(V_{GS}-V_{th})^2(1+\lambda V_{DS})$$

with

$$k=10^{-3}, V_{th}=1 \text{ and } \lambda=0.2 \text{ (use output conductance } g_o=\lambda I_D)$$

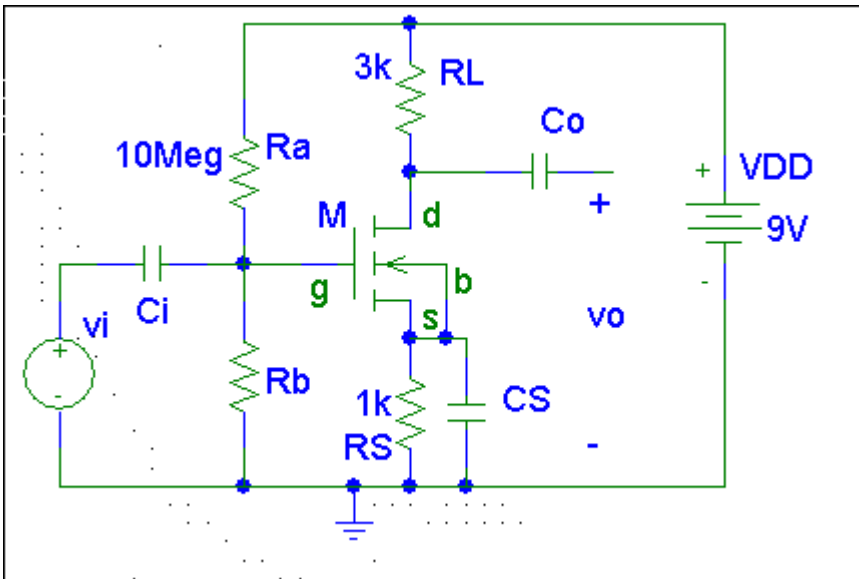
- Determine V_{DS} at bias.
- Determine V_{GS} and R_b at bias.
- With frequencies such that all capacitors shown act as shorts, give the small signal voltage gain, v_o/v_i .



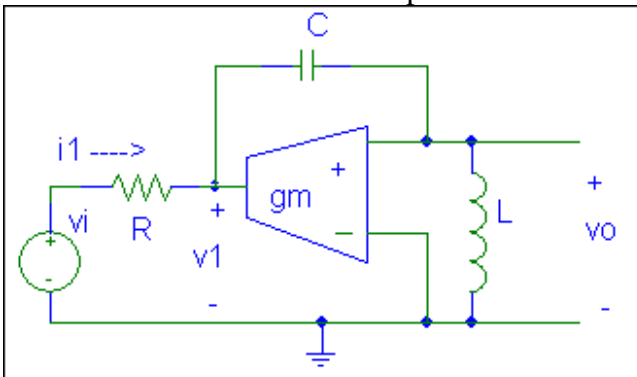2. 7 points

An Operational Transconductance Amplifier (OTA) is described by the property that no current flows into the input (+ & - terminals) and has output current (directed into the OTA) as $i_o=g_m(v_+ - v_-)$ where g_m is the transconductance.

For the following OTA circuit find the open circuit voltage gain, $v_o(s)/v_i(s)$, and discuss the possibility of this forming an oscillator. [note that the node voltage V_1 is labelled for convenience and should not be part of the answer].



3. 6 points



A tunnel diode is described by its current i_d versus voltage v_d by the equation

$$i_d = 0.1v_d(v_d^2 - 10.5v_d + 30)$$

for which the derivative is $di_d/dv_d = 0.3(v_d - 2)(v_d - 5)$. It has a load current y given by $y = m \cdot v_d + Y_0$

These curves are plotted below [followed by the bottom figure giving detail near the intersect points.

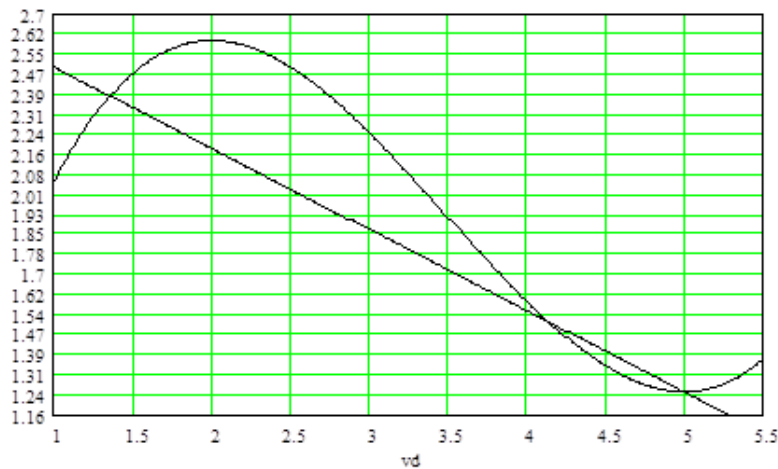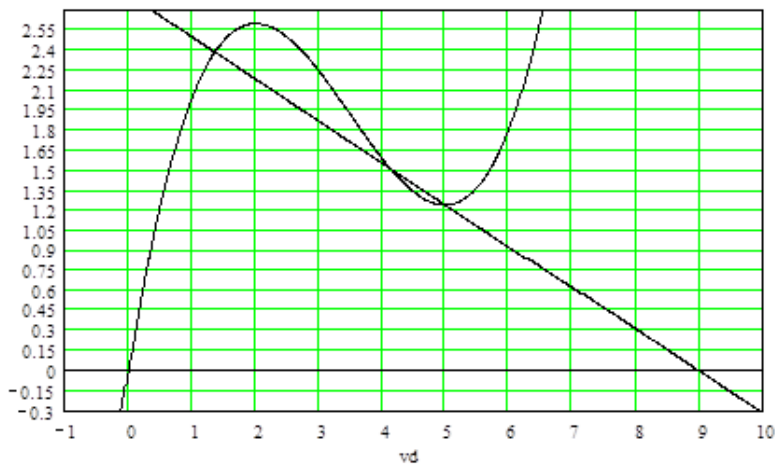- Determine m and Y_0 for the load line (given that it passes through the local minimum of i_d at $v_d = 5$).
- Give the current and voltage values at the middle intersect point.
- Determine the small signal conductance at the middle intersect point.



solutions, circuits 2018 spring

#1. a) by KVL: $V_{DS} = V_{DD} - (R_L + R_S)I_D = 9 - (3+1) \times 10^3 \times 1 \times 10^{-3} = 9 - 4 = 5V = V_{DS}$


b) $I_D = 1 \times 10^{-3} = 1 \times 10^{-3} (V_{GS} - 1)^2 (1 + 0.2 \times 5) \Rightarrow 1 = (V_{GS} - 1)^2 \times 2 \Rightarrow V_{GS} = 1 \pm \sqrt{2}$
 $\Rightarrow V_{GS} = 1 + \sqrt{2}$ (use + sign as $V_{GS} > 1$ for $I_D > 0$)

for R_b : $V_G = \frac{R_b}{R_a + R_b} \cdot V_{DD} = V_{GS} + R_S I_D = 1 + \frac{1}{\sqrt{2}} + 10^3 \times 10^{-3} = 2 + \frac{1}{\sqrt{2}} = 2.707$

$\Rightarrow (2 + \frac{1}{\sqrt{2}})(R_a + R_b) = R_b \times 9 \Rightarrow (2 + \frac{1}{\sqrt{2}})R_a = (7 - \frac{1}{\sqrt{2}})R_b$

$\Rightarrow R_b = (\frac{2\sqrt{2}+1}{7\sqrt{2}-1})R_a = \frac{3.828}{8.90}R_a = 0.434R_a \Rightarrow R_b = 4.134M\Omega$

c) small signal equivalent circuit

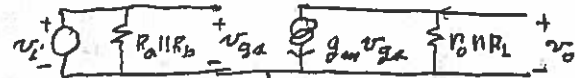


$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{2I_D}{(V_{GS} - V_{th})} = \frac{2 \times 10^{-3}}{(1 + \frac{1}{\sqrt{2}} - 1)} = \frac{2 \times \sqrt{2} \times 10^{-3}}{1} = 2.83 \times 10^{-3} S$

assumption of prob: $g_{o1} = \lambda I_D = 0.2 \times 10^{-3} = 2 \times 10^{-4} \Rightarrow Y_{o1} = 10^4 / 2 = 5 \times 10^3$

more accurate: $g_{o2} = \frac{\partial I_D}{\partial V_{DS}} = \lambda (V_{GS} - V_{th})^2 = 10^{-3} (1 + \frac{1}{\sqrt{2}} - 1)^2 \times 0.2 = \frac{1}{2} \times 2 \times 10^{-4} = 1 \times 10^{-4} \Rightarrow Y_{o2} = 10 \times 10^3$

$\therefore v_o/v_i = -g_m (R_D || R_L) \approx -2.83 \times 10^{-3} \times (\frac{5 \times 3}{5+3}) \times 10^3 = -2.83 \times \frac{15}{8} = -5.3$ or $-2.83 \times \frac{3 \times 10}{3+10} = -6.53$

#2 Equivalent circuit

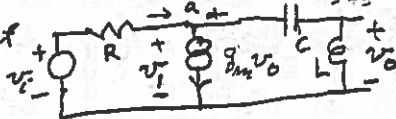

KCL @ a: $G(v_i - v_o) - g_m v_o + sC(v_o - v_i) = 0, G = 1/R \Rightarrow v_i$ in terms of $v_o \Rightarrow (G - g_m)v_o = (G + sC)v_i$

$\Rightarrow v_i = [Gv_i + (sC - g_m)v_o] / [G + sC]$ also by voltage divider $v_o = \frac{sC}{sC + 1/R} v_i$

$\Rightarrow v_i = \frac{(s^2 LC + 1)v_o}{s^2 LC} \Rightarrow (s^2 LC + 1)(G + sC)v_o = s^2 LC [Gv_i + (sC - g_m)v_o]$

$\Rightarrow \frac{v_o}{v_i} = \frac{s^2 LC G}{[s^2 LC(G + g_m) + sC + G]} = \frac{s^2 LC}{LC(1 + g_m R)s^2 + sRC + 1}$

\Rightarrow oscillator if $RC = 0 \Rightarrow R = 0$ (as $C = 0 \Rightarrow v_o = 0$), to get a pole @ $LCs^2 + 1 = 0 \Rightarrow \omega_0 = 1/\sqrt{LC}$

#3 a) For the load line need 2 points: $i = 0 @ v_D = 9, @ v_D = 5, i = 0.1 \times 5(25 - 5 \times 5 + 30) = 1.25$

$y = 0 = m \times 9 + Y_0, y = 1.25 = m \times 5 + Y_0$ subtract $1.25 = m(5 - 9) \Rightarrow m = -1.25/4 = -0.3125 = m$

$\Rightarrow Y_0 = +1.25/4 \times 9 = 2.8125 = Y_0 = 45\% \mu$

b) @ the middle intersect point $0.1 \times 5 (v_D^2 - 10.5v_D + 30) = -0.3125v_D + 2.8125$

which is a cubic with a known zero @ $v_D = 5 \Rightarrow v_D^3 - 10.5v_D^2 + 33.125v_D - 28.125 = (v_D - 5)(v_D^2 + av_D + b)$

equating coefficients $-5b = -28.125, -10.5 = -5 + a \Rightarrow a = -5.5, b = 5.625$

$v_{D2,3} = \frac{5.5 \pm \sqrt{(5.5)^2 - 4 \times 5.625}}{2} = \frac{5.5 \pm \sqrt{30.25 - 22.5}}{2} = \frac{5.5 \pm 2.674}{2} = 4.142$ or 1.358

\therefore middle $v_D = 4.142$ and $i = -0.3125 \times 4.142 + 2.8125 = 1.518 = i_D$ (from curve we see $v_D \times 4.2, i_D = 1.5$)

c) $g = \frac{\partial i_D}{\partial v_D} = 0.3(v_D - 2)(v_D - 5) \Big|_{v_D = 4.142} = 0.3(4.142 - 2)(4.142 - 5) = -0.6275$

intersect

(Using guess from curve = $0.3(4.2 - 2)(4.2 - 5) = 0.3 \times 2.2 \times (-0.8) = -0.528$)