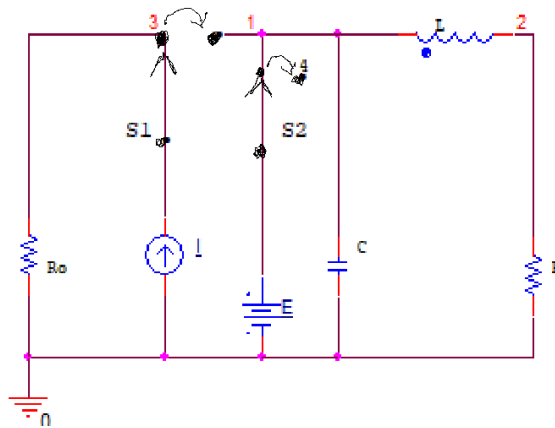


ECE Written Qualifying Examination, Circuits Spring 2019

1. 7 points

The following circuit is assumed to have existed for all time. At  $t=0$  the switch  $S1$  switches from node 3 to node 1 (connecting  $I$  to the RLC circuit) and  $S2$  opens (switching from node 1 to node 4, thus disconnecting  $E$ ).  $I$  and  $E$  are constant, DC, current and voltage, respectively;  $R$ ,  $R_0$ ,  $L$  and  $C$  are positive element values.

- (3 points) Set up the (second order) differential equation for  $v_1(t)$  for  $t>0$  [where  $v_1$  is the capacitor node voltage measured with respect to ground].
- (3 points) Find the following capacitor voltage and current values immediately before and after switching,  $v_1(0^-)$ ,  $Cdv_1/dt(0^-)$  and  $v_1(0^+)$ ,  $Cdv_1/dt(0^+)$ .
- (1 point) Give the final values  $v_1(\infty)$  and inductor current  $i_L(\infty)$  [entering the dot].




2. 6 points

In the following bridge circuit the meter in the center is an amp-meter with input resistance of  $0 \text{ Ohms}$ .  $V_i$  is the voltage of the voltage source and the four branches are described by their admittances,  $y_i$ ,  $i=1, 2, 3, 4$ . The current  $I_m$  in the meter is known to be given by

$$I_m = [(y_2 \cdot y_3 - y_1 \cdot y_4) / (y_1 + y_2 + y_3 + y_4)] V_i$$

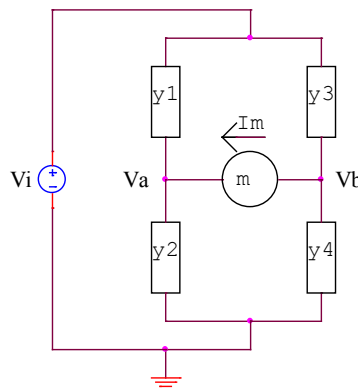- (3 points) Find the relationship between the  $y_i$  such that the bridge is in balance, that is when  $I_m=0$ .
- (3 points) If  $y_1$  at balance is perturbed to become  $y_5=y_1+\Delta y_1$  [where  $y_1$  is as in a)] and  $y_2$  and  $y_3$  are unperturbed, find the perturbation  $\Delta y_4$  of  $y_4$  such that  $y_4+\Delta y_4$  returns the bridge to balance.



3. 7 points

When the following NMOS transistor is in saturation (that is when  $V_{DS} \geq V_{GS} - V_{th}$ ) its drain current is described by ( $k$  and the threshold voltage  $V_{th}$  are both positive)


$$I_D = k(V_{GS} - V_{th})^2 \quad [\text{for NMOS}]$$

Assume also that the PMOS is completely complementary, that is (with the same  $k$  and  $V_{th}$ ) so that

$$I_S = k(V_{SG} - V_{th})^2 \quad [\text{for PMOS}]$$

(here the source current  $I_S$  and the drain current  $I_D$  are taken as positive when going into the source, S, and the drain, D, respectively)

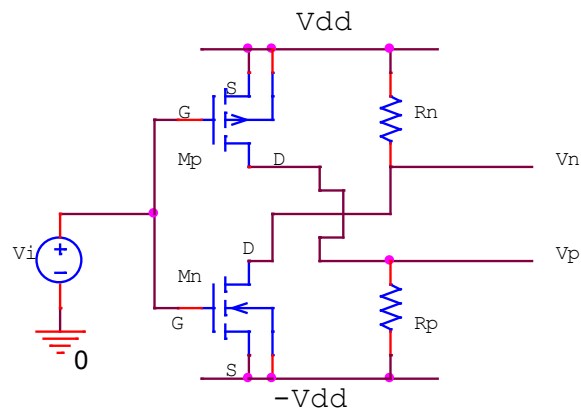The bias voltage  $V_{dd}$  is large enough to make the circuit operational [note the presence of the negative bias].




a) (3 points) When the input voltage is zero,  $V_i = 0$ , find the maximum resistance value,  $R_n = R_{max}$  [in terms of  $k$ ,  $V_{th}$  and  $V_{dd}$ ], such that the NMOS transistor is in saturation.

b) (3 points) Again at  $V_i = 0$  and when  $R_n$  and  $R_p$  are both smaller than  $R_{max}$ , find the output difference voltage,  $V_{diff} = V_n - V_p$ , (again in terms of  $k$ ,  $V_{th}$  and  $V_{dd}$ ) [  $V_n$  and  $V_p$  are measured with respect to ground ].

c) (1 point) Is it possible to design the circuit to obtain  $V_{diff} = 0$  when  $V_i = 0$ ? Explain your answer.

#1. The circuit for  $t > 0$  is

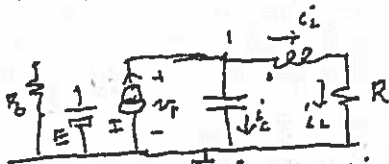

a) then KCL:  $I = i_C + i_L$

$$\Rightarrow i_L = I - C \frac{dv_C}{dt}$$

$$\text{KVL: } v_C = L \frac{di_L}{dt} + R i_L$$

$$\Rightarrow C \frac{dv_C}{dt} + RC \frac{dv_C}{dt} + \frac{1}{L} v_C = \frac{RI}{L}$$

$$+ C \frac{dv_C}{dt} = 0 - \frac{di_L}{dt} = -\frac{1}{L} (v_C - R i_L) = -\frac{1}{L} v_C + \frac{R}{L} (I - C \frac{dv_C}{dt})$$

b) as the original configuration is at a steady DC state at  $t = 0^-$ :  $v_C(0^-) = E$ ,  $C \frac{dv_C(0^-)}{dt} = i_L(0^-) = 0$   
 after the switch change  $v_C$  &  $i_L$  can not jump (to avoid infinite) so  $v_C(0^+) = v_C(0^-)$ ,  $i_L(0^+) = E/R = i_L(0^-) \Rightarrow i_C(0^+) = I - i_L(0^+)$

$$\therefore v_C(0^+) = E, C \frac{dv_C(0^+)}{dt} = I - E/R$$

c) From the above figure  $i_C(\infty) = 0 \Rightarrow i_L(\infty) = I$  &  $v_L(\infty) = 0 \Rightarrow v_C(\infty) = R i_L(\infty) = RI$

#2. a) at balance  $i_M = 0 \Rightarrow y_2 y_3 = y_1 y_4$

b) with the new balance  $y_2 y_3 = (y_1 + \Delta y_1)(y_4 + \Delta y_4) = y_1 y_4 + [y_1 \Delta y_4 + y_4 \Delta y_1 + \Delta y_1 \Delta y_4]$

$$\Rightarrow [\cdot] \text{ term} = 0 \Rightarrow 0 = y_4 \Delta y_1 + (y_1 + \Delta y_1) \Delta y_4 \Rightarrow \Delta y_4 = \frac{-\Delta y_1 y_4}{y_1 + \Delta y_1}$$

#3. a)  $V_{GS_n} = V_{DD}$ ,  $V_{DS_n} = 2V_{DD} - R_{n,max} \cdot k_n (V_{GS_n} - V_{th})^2 \geq V_{GS_n} - V_{th}$

$$\Rightarrow 2V_{DD} - R_{n,max} \cdot k_n (V_{DD} - V_{th})^2 = V_{DD} - V_{th}$$

$$\Rightarrow V_{DD} + V_{th} = R_{n,max} \cdot k_n (V_{DD} - V_{th})^2 \Rightarrow R_{n,max} = \frac{V_{DD} + V_{th}}{k_n (V_{DD} - V_{th})^2} = \frac{R_{n,max}}{k_n (V_{DD} - V_{th})}$$

b)  $V_m = V_{DD} - R_m \cdot k_n (V_{DD} - V_{th})^2$ ,  $V_p = R_p \cdot k_n (V_{DD} - V_{th})^2 + (-V_{DD})$

$$\Rightarrow V_m - V_p = V_{DD} - R_m \cdot k_n (V_{DD} - V_{th})^2 - (-V_{DD}) - R_p \cdot k_n (V_{DD} - V_{th})^2$$

$$= 2V_{DD} - (R_m + R_p) k_n (V_{DD} - V_{th})^2 = V_{diff}$$

c) we need  $V_m - V_p = 0 \Rightarrow (R_m + R_p) \cdot k_n (V_{DD} - V_{th})^2 = 2V_{DD}$  or  $R_m + R_p = \frac{2V_{DD}}{k_n (V_{DD} - V_{th})^2}$

The maximum  $(R_m + R_p)$  can be

$$i_{max}(R_m + R_p) = 2 R_{n,max} = \frac{2 V_{DD}}{k_n (V_{DD} - V_{th})^2} + \frac{2 V_{th}}{k_n (V_{DD} - V_{th})^2}$$

as this exceeds by  $\frac{2 V_{th}}{k_n (V_{DD} - V_{th})^2}$  the amount needed to force  $V_m - V_p = 0$

we can choose  $R_s = R_n = R_p = R_{n,max} - \frac{V_{th}}{k_n (V_{DD} - V_{th})^2}$  to make  $V_m - V_p = 0$