

Digital Logic Design

ENEE 244-010x

Lecture 13

Announcements

- HW 6 due on Wednesday, 10/28

Agenda

New Topic: MSI Components

- Today:
 - Binary Adders and Subtractors (5.1, 5.1.1)
 - Carry Lookahead Adders (5.1.2, 5.1.3)

Scale of Integration

- Scale of Integration = Complexity of the Chip
 - SSI: small-scale integrated circuits, 1-10 gates
 - MSI: medium-scale IC, 10-100 gates
 - LSI: large scale IC, 100-1000 gates
 - VLSI: very large-scale IC, 1000+ gates
 - Today's chip has millions of gates on it.
- MSI components: adder, subtracter, comparator, decoder, encoder, multiplexer.

Scale of Integration

- LSI technology introduced highly generalized circuit structures known as programmable logic devices (PLDs).
 - Can consist of an array of and-gates and an array of or-gates. Must be modified for a specific application.
 - Modification involves specifying the connections using a hardware procedure. Procedure is known as programming.
- Three types of programmable logic devices:
 - Programmable read-only memory (PROM)
 - Programmable logic array (PLA)
 - Programmable array logic (PAL)

MSI Components

Binary Full Adder

x_i	y_i	c_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Finding a Simplified Circuit

0	1	0	1
1	0	1	0

0	0	1	0
0	1	1	1

Corresponding minimal sums:


$$s_i = \bar{x}_i \bar{y}_i c_i + \bar{x}_i y_i \bar{c}_i + x_i \bar{y}_i \bar{c}_i + x_i y_i c_i$$

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

We can simplify the sum for s_i by using xor:

$$s_i = c_i \oplus x_i \oplus y_i$$


Realization of Full Binary Adder

 

What about many bits?

- Consider addition of two binary numbers, each consisting of n bits.
- Direct approach: Write a truth table with 2^{2n} rows corresponding to all the combinations of values and specifying the values of the sum bits. Then find a minimal combinational network.
- This will be intractable.

Parallel (ripple) Binary Adder

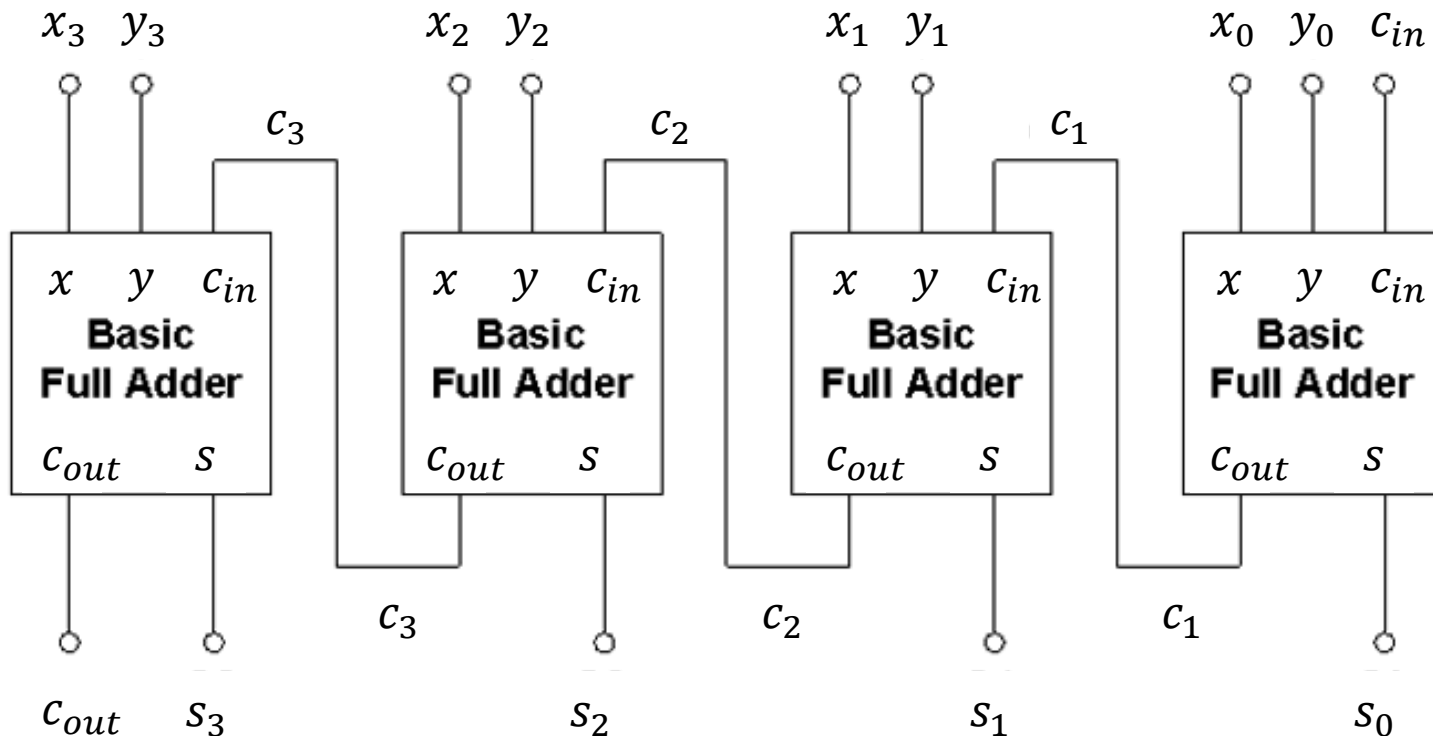

Why is it called “ripple” adder?
Recall—signed binary numbers,
final carry-out may signal overflow.

Binary Subtractors

Compute: $x_i - y_i$.

b_i is a borrow-in bit from previous bit-order position.

b_{i+1} is a borrow-out bit.

x_i	y_i	b_i	b_{i+1}	d_i
0	0	0	0	0
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		


Binary Subtractors

Compute: $x_i - y_i$.

b_i is a borrow-in bit from previous bit-order position.

b_{i+1} is a borrow-out bit.

x_i	y_i	b_i	b_{i+1}	d_i
0	0	0	0	0
0	0	1	1	1
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

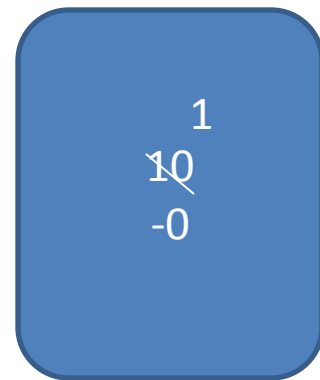


Binary Subtractors

Compute: $x_i - y_i$.

b_i is a borrow-in bit from previous bit-order position.

b_{i+1} is a borrow-out bit.

x_i	y_i	b_i	b_{i+1}	d_i
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 


Binary Subtractors

Compute: $x_i - y_i$.

b_i is a borrow-in bit from previous bit-order position.

b_{i+1} is a borrow-out bit.

x_i	y_i	b_i	b_{i+1}	d_i
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 

Binary Subtractors

Compute: $x_i - y_i$.


b_i is a borrow-in bit from previous bit-order position.

b_{i+1} is a borrow-out bit.


x_i	y_i	b_i	b_{i+1}	d_i
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Finding a Simplified Circuit

 
$$d_i = b_i \oplus x_i \oplus y_i \text{ (Same as sum in adder)}$$
$$b_{i+1} = \bar{x}_i y_i + \bar{x}_i b_i + y_i b_i$$



A better approach using 2's complement

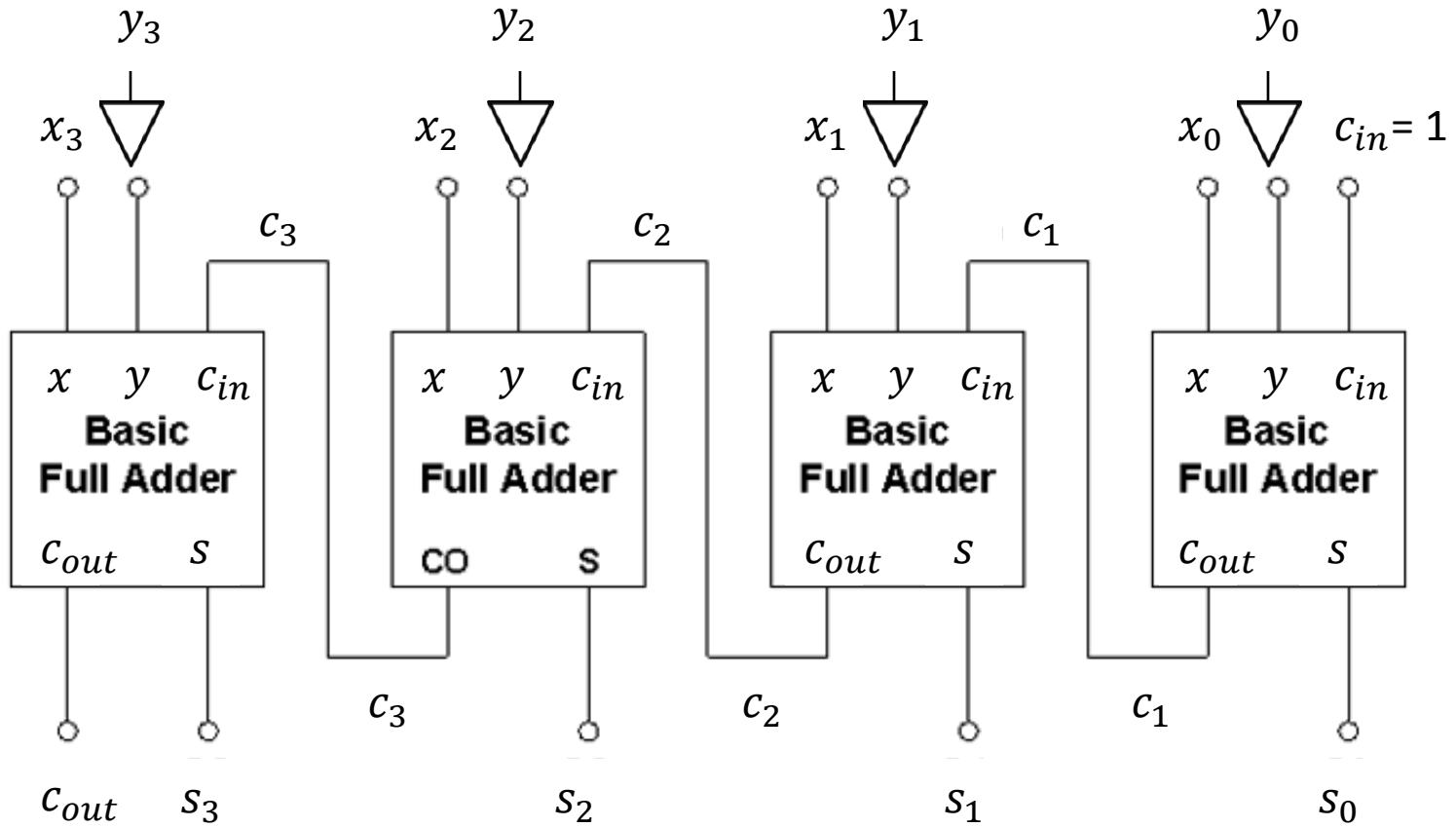

Parallel Adder/Subtractor

 

Carry Lookahead Adder

- Ripple effect:
 - If a carry is generated in the least-significant-bit the carry must propagate through all the remaining stages.
 - Assuming two-levels of logic are need to propogate the carry through each of the next higher-order stages. Delay is $2n$.
- Must speed up propagation of the carries. Adders designed with this consideration in mind are called **high-speed adders**.

Carry Lookahead Adder

- Consider $c_{i+1} = x_i y_i + x_i c_i + y_i c_i$
$$= x_i y_i + (x_i + y_i) c_i$$
- The first term $x_i y_i$ is called the **carry-generate function** since it corresponds to the formation of a carry at the i -th stage.
- The second term $(x_i + y_i) c_i$ corresponds to a previously generated carry c_i that must propagate past the i -th stage to the next stage.
- The $(x_i + y_i)$ part of this term is called the **carry-propagate function**.
- Carry-generate function will be denoted by g_i , carry-propagate function will be denoted by p_i .

Carry Lookahead Adder

$$g_i = x_i y_i$$

$$p_i = x_i + y_i$$

$$c_{i+1} = g_i + p_i c_i$$

Using this general result, the output carry at each of the stages can be written in terms of the g 's, p 's and initial input carry c_0 .

Carry Lookahead Adder

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 c_1$$

$$= g_1 + p_1 (g_0 + p_0 c_0)$$

$$= g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 c_2$$


$$= g_2 + p_2 (g_1 + p_1 g_0 + p_1 p_0 c_0)$$

$$= g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$


$$c_{i+1} = g_i + p_i g_{i-1} + p_i p_{i-1} g_{i-2} + \cdots + p_i p_{i-1} \cdots p_1 g_0 \\ + p_i p_{i-1} \cdots p_0 c_0$$

Why is this a good idea? Do we save on computation?

Carry Lookahead Adder

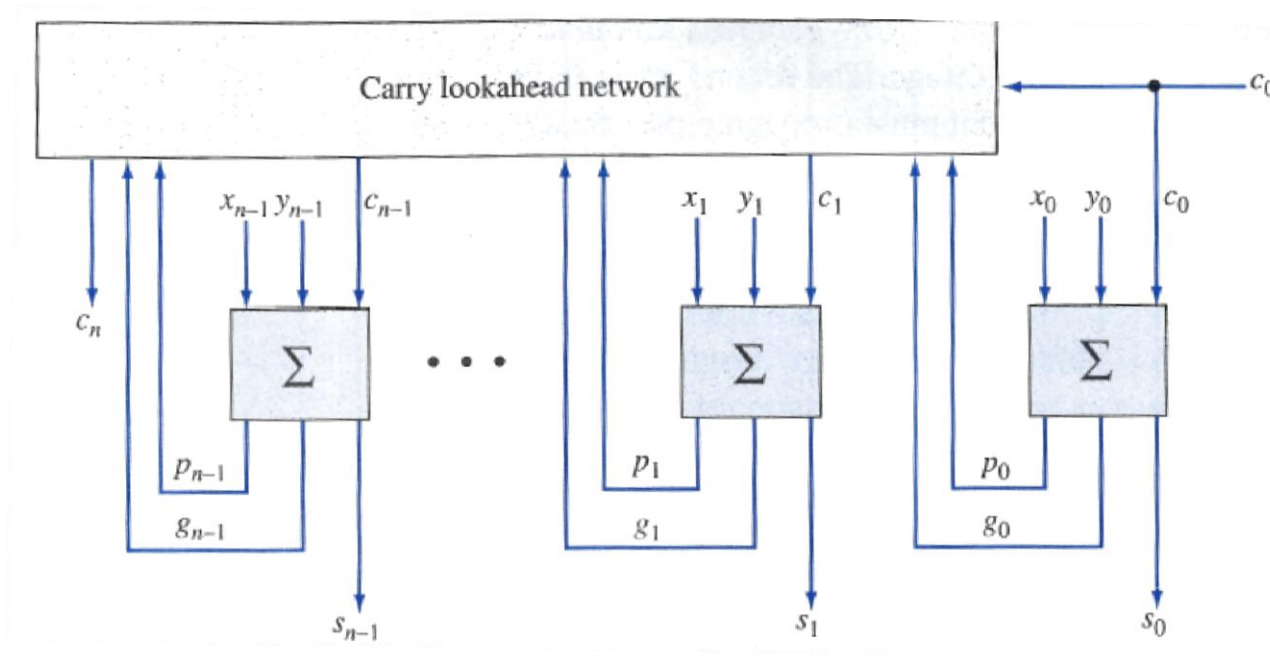

Carry Lookahead Adder

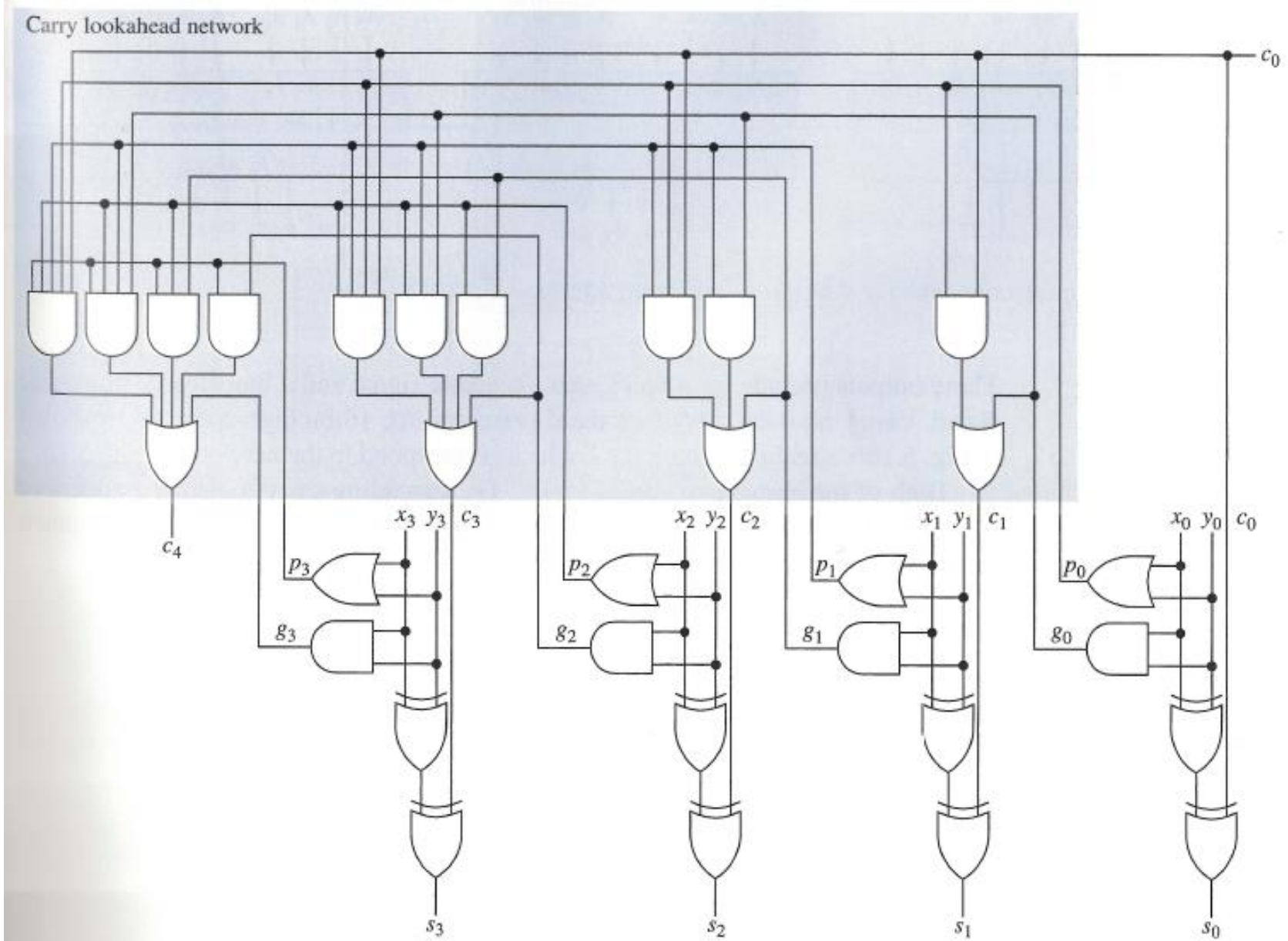

Carry Lookahead Adder

- What is the delay?
 - One level of logic to form g 's, p 's
 - Two levels of logic to propagate through the carry lookahead
 - One level of logic to have the carry effect a sum output.
 - Total: 4 units of time.
- Delay of 4-bit ripple-adder?
 - 2 levels of logic for each c_1, c_2, c_3, c_4
 - 8 levels of logic

Large High-Speed Adders


- The carry lookahead network can very large as the number of bits increases.
- Approach: Divide bits of the operands into blocks, use carry lookahead adders for each block. Cascade the adders for the blocks.
- Ripple carries occur between the cascaded adders.

Another Approach to Large High-Speed Adders

- Carry lookahead generators that generate the carry of an entire block.
- Assume 4-bit blocks.
- For each block, 4-bit carry lookahead generator outputs:

$$G = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0$$
$$P = p_3p_2p_1p_0$$

Carry Lookahead Generator

 

Large High-Speed Adders

