 


Latches and Flip-Flops

ENEE 244-010x

SR-Latch




Logic Diagram

| Inputs | | Outputs | |
|--------|---|---------|-------------|
| S | R | Q^+ | \bar{Q}^+ |
| 0 | 0 | Q | \bar{Q} |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0^* | 0^* |


*Unpredictable behavior will result if inputs return to 0 simultaneously

Truth Table

 


Symbol

Gated SR-Latch

 

| Inputs | | | Outputs | |
|--------|---|---|---------|-------------|
| S | R | C | Q^+ | \bar{Q}^+ |
| 0 | 0 | 1 | Q | \bar{Q} |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1^* | 1^* |
| X | X | 0 | Q | \bar{Q} |

 *Unpredictable behavior will result if S and R return to 0 simultaneously or C returns to 0 while S and R are 1




(c)


Decoders, Encoders and Multiplexers

ENEE 244-010x


Gated D-Latch

 


| Inputs | | Outputs | |
|--------|---|---------|-------------|
| D | C | Q^+ | \bar{Q}^+ |
| 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |
| X | 0 | Q | \bar{Q} |

 

Master-Slave SR Flip-Flop

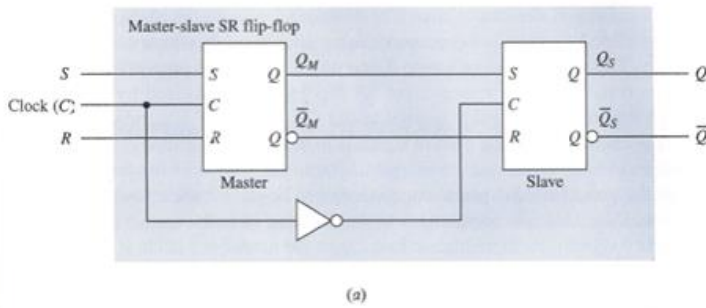


| Inputs | | | Outputs | |
|--------|---|---|-----------|-------------|
| S | R | C | Q^+ | \bar{Q}^+ |
| 0 | 0 | | Q | \bar{Q} |
| 0 | 1 | | 0 | 1 |
| 1 | 0 | | 1 | 0 |
| 1 | 1 | | Undefined | Undefined |
| X | X | 0 | Q | \bar{Q} |

 

Decoders, Encoders and Multiplexers

ENEE 244-010x

Master-Slave JK Flip-Flop

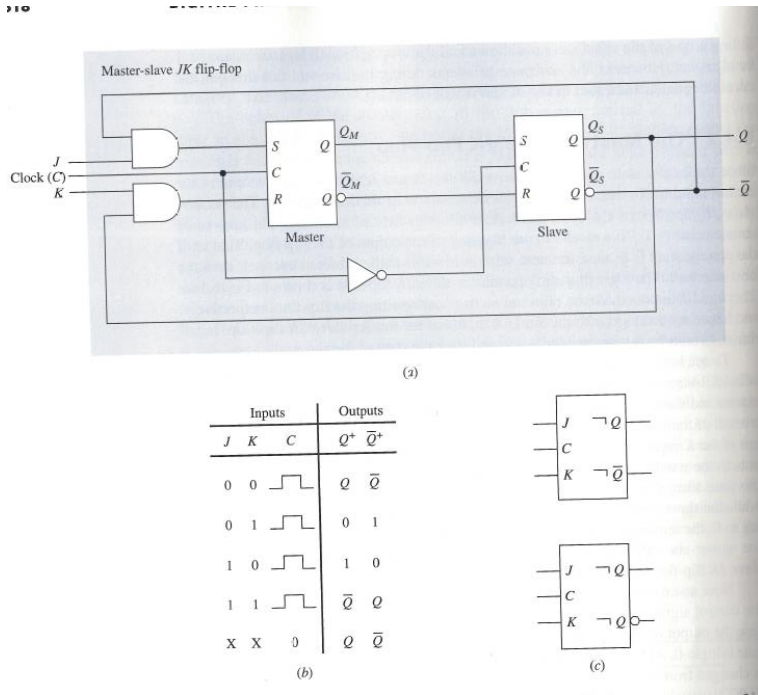

Positive Edge Triggered D Flip-Flop

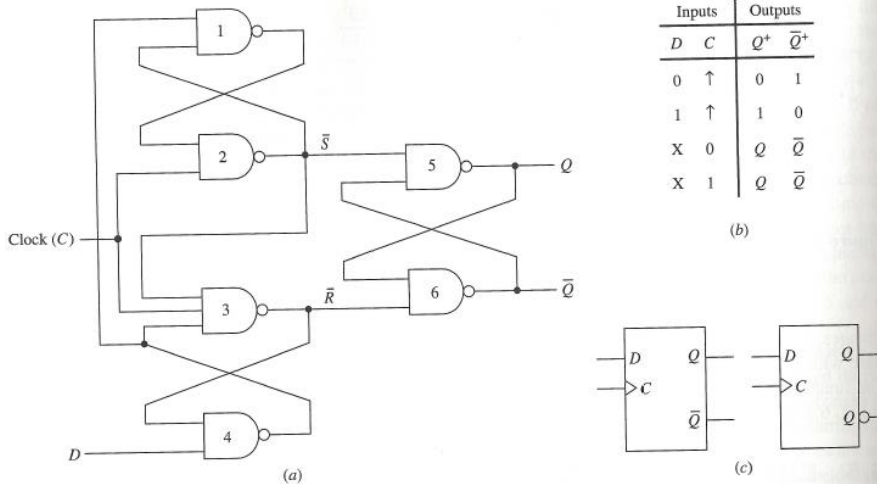


Figure 6.18 Positive-edge-triggered *D* flip-flop. (a) Logic diagram. (b) Function table where Q^+ denotes the output Q in response to the inputs. (c) Two logic symbols.

Decoders, Encoders and Multiplexers

ENEE 244-010x

Positive Edge-Triggered T Flip-Flop

