

Digital Logic Design

ENEE 244-010x

Lecture 18


Announcements

- Homework 8 up on course webpage. Due Monday, 11/23

Agenda


- Last time:
 - The Basic Bistable Element (6.1)
 - Latches (6.2)
 - Timing Considerations (6.3)
- This time:
 - Review of 6.2-6.3
 - Master-Slave Flip-Flops (6.4)
 - Edge-Triggered Flip-Flops (6.5)
 - Characteristic Equations (6.6)

Review--The SR Latch

 


Inputs		Outputs	
S	R	Q^+	\bar{Q}^+
0	0	Q	\bar{Q}
0	1	0	1
1	0	1	0
1	1	0^*	0^*

 *Unpredictable behavior will result if inputs return to 0 simultaneously



Q^+, \bar{Q}^+ indicates the response of the latch at the Q, \bar{Q} output terminals as a consequence of applying the various inputs. Q^+ is called the next state of the latch.

Review--The Gated SR Latch

 


(a)

Inputs			Outputs	
S	R	C	Q^+	\bar{Q}^+
0	0	1	Q	\bar{Q}
0	1	1	0	1
1	0	1	1	0
1	1	1	1*	1*
X	X	0	Q	\bar{Q}


*Unpredictable behavior will result if S and R return to 0 simultaneously or C returns to 0 while S and R are 1

(b)

 


(c)

Review--The Gated D Latch

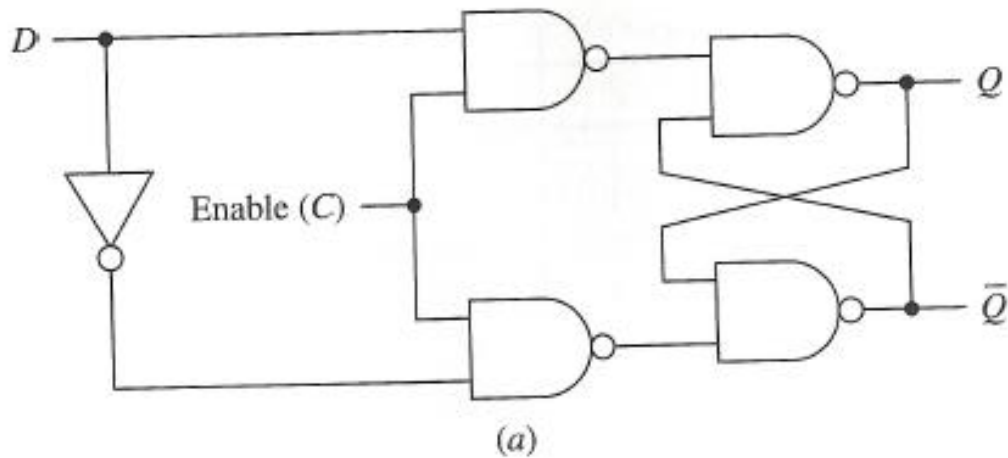

Inputs		Outputs	
D	C	Q^+	\bar{Q}^+
0	1	0	1
1	1	1	0
X	0	Q	\bar{Q}

(b)

 

Propagation Delays

- The propagation delay is the time it takes a change in an input signal to produce a change in an output signal.
- Propagation delay from low to high: t_{pLH}
- Propagation delay from high to low: t_{pHL}

In general, these may be different.


 


Figure 6.7 Propagation delays in an SR latch.


Timing Diagram

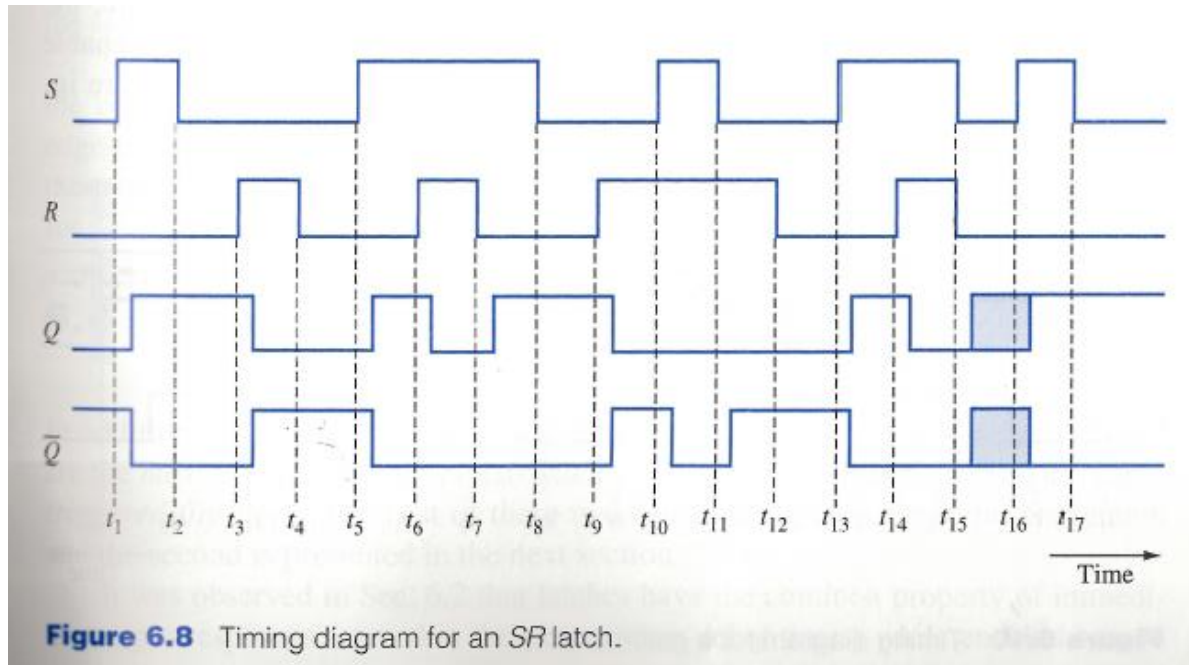- Propagation delays from high-low, low-high assumed equal.
- When $S = R = 1$, both Q, \bar{Q} become 0.
- t_{15} , signals on S, R are simultaneously changed from 1 to 0.
 - Response of latch is unpredictable. Can be in 0-state, 1-state or metastable state.
 - Application of 1 on the set input terminal returns the latch to predictable.




Minimum Pulse Width

 - Another specification stated by the manufacturers of latches is that of a minimum pulse width $t_{w(min)}$.
 - Minimum amount of time a signal must be applied in order to produce a desired result.
- Failure to satisfy the constraint may cause unintended change or have the latch enter its metastable state.



Setup and Hold Times

 - Consider timing diagram for a gated D latch
- Q-output follows the input signal at D whenever the enable signal C = 1.
- When C = 0, changes are ignored.



- Consider times t_3, t_6, t_{11}, t_{14} .
 - C is returned to 0. Output latches onto its current state.
 - To guarantee latching action: constraint is placed on D signal. Must not change right before and after C goes from 1 to 0.
- Setup time: minimum time t_{su} that D signal must be held fixed before the latching action.
- Hold time: minimum time t_h that D signal must be held fixed after the latching action.

Unpredictable Response in a gated D latch

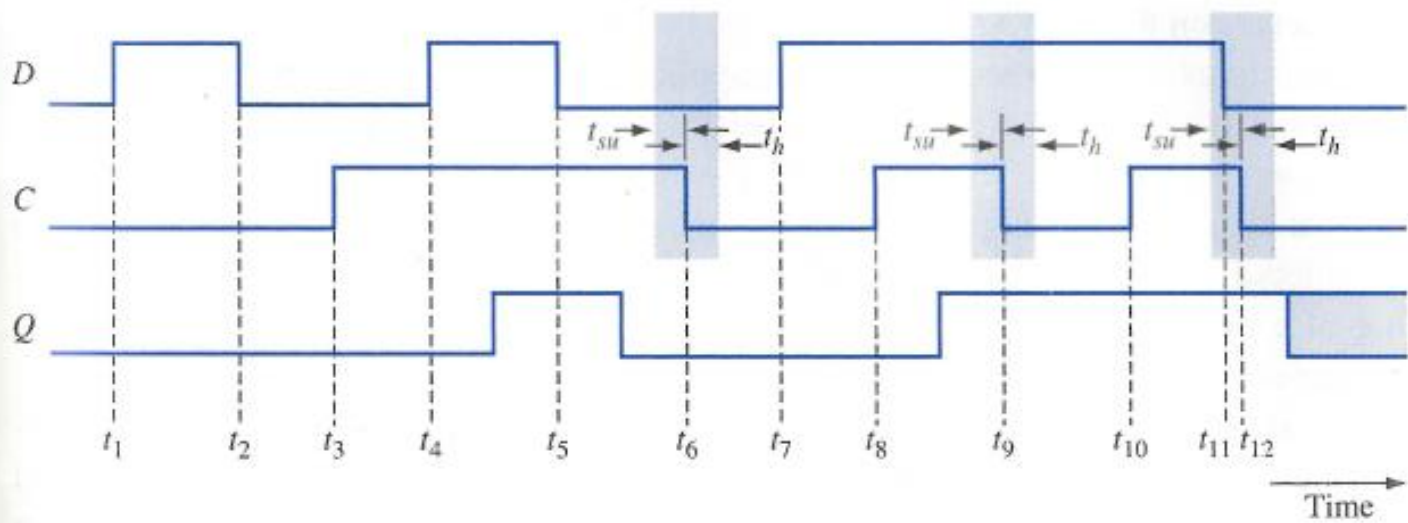



Figure 6.11 Illustration of an unpredictable response in a gated *D* latch.

Master-Slave Flip-Flops (Pulse Triggered Flip-Flops)


- Aside from latches, two categories of flip-flops.
 - Master-slave flip-flops (pulse-triggered flip-flops)
 - Edge-triggered flip-flops
- Latches have immediate output response (known as transparency)
- May be undesirable:
 - May be necessary to sense the current state of a flip-flop while allowing new state information to be entered.

Master-Slave SR Flip-Flop

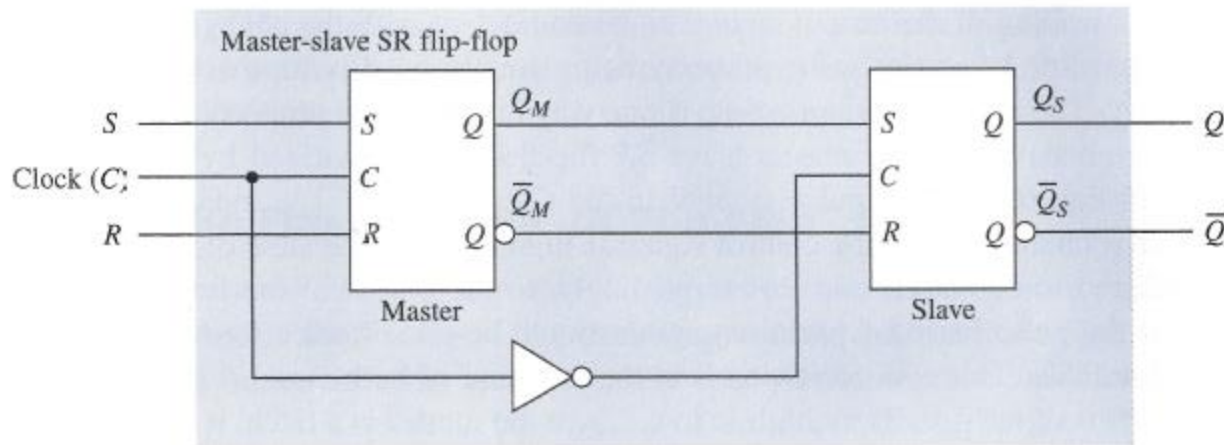- Two sections, each capable of storing a binary symbol.
- First section is referred to as the master and the second section as the slave.
- Information is entered into the master on one edge or level of a control signal and is transferred to the slave on the next edge or level of the control signal.
- Each section is a latch.




Master-Slave SR Flip-Flop

 


- $C = 0$:
 - Master is disabled. Any changes to S,R ignored.
 - Slave is enabled. Is in the same state as the master.
- $C = 1$:
 - Slave is disabled (retains state of master)
 - Master is enabled, responds to inputs. Changes in state of master are not reflected in disabled slave.
- $C = 0$:
 - Master is disabled.
 - Slave is enabled and takes on new state of the master.
- Important: For short periods during rising and falling edges, both master and slave are disabled.

Master-Slave SR Flip-Flop

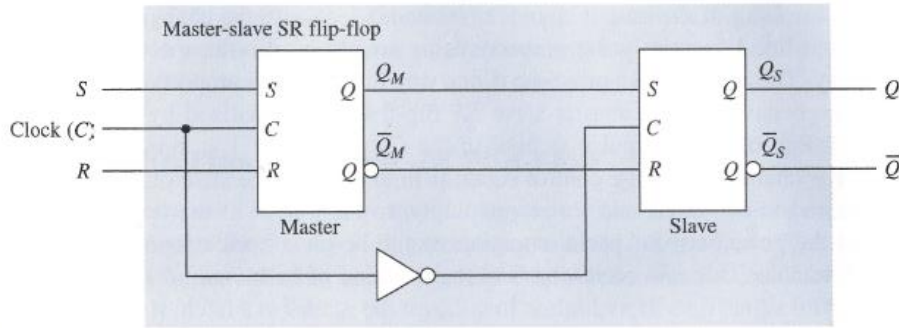



(a)

 

(b)

Inputs			Outputs	
S	R	C	Q^+	\bar{Q}^+
0	0	1	Q	\bar{Q}
1	1	1	0	1
1	0	1	1	0
1	1	1	Undefined	Undefined
X	X	0	Q	\bar{Q}

(c)

  

(d)


Pulse symbol indicates master enabled when $C = 1$ and state of master transferred to slave at the end of the pulse period.

Slave only takes on state of the master at t_4 .

Postponed output indicator: output change postponed until end of pulse

If $S, R = 1$ when control signal goes from high to low we are in an unpredictable state. Can cause metastable state.

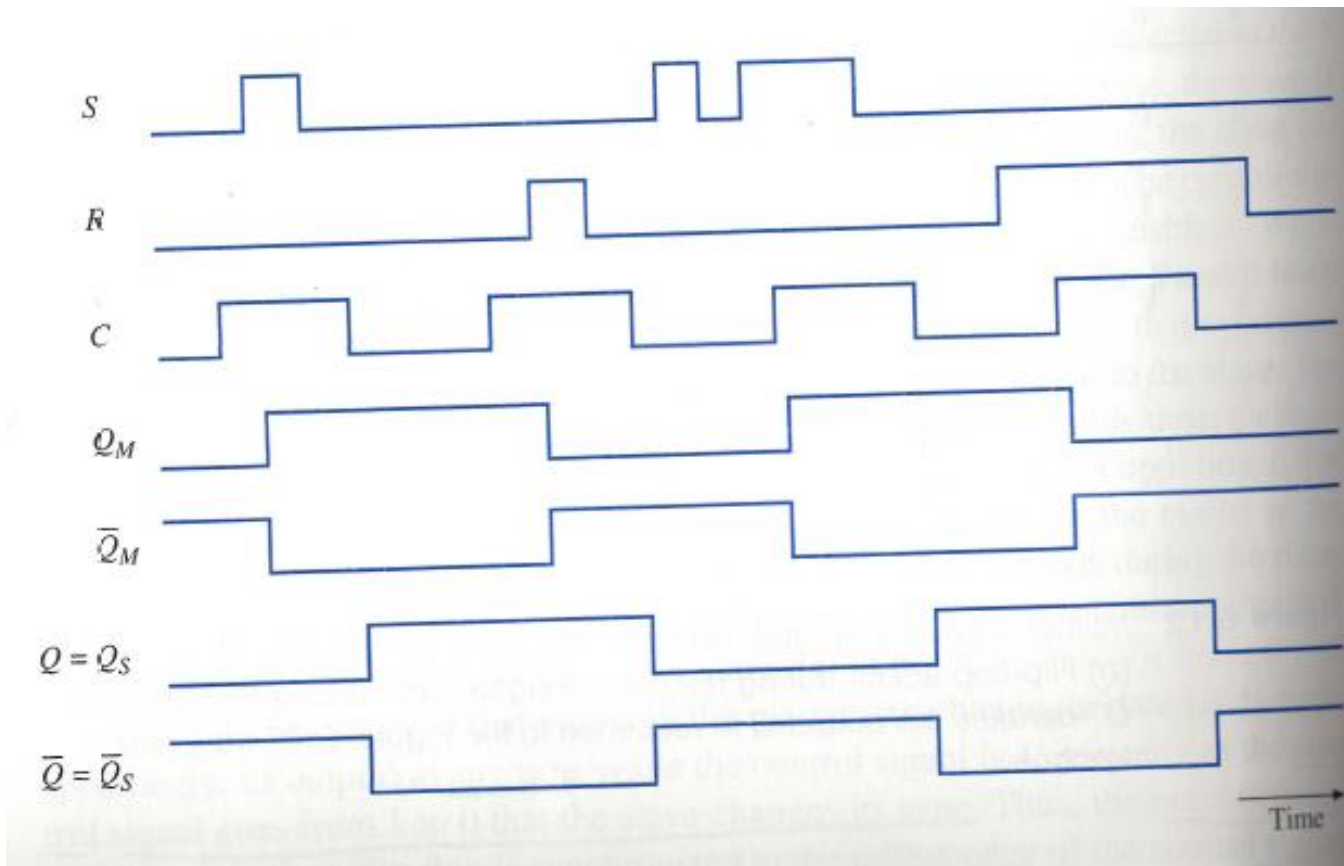
Timing Diagram for Master-Slave SR flip-flop



Master-Slave JK Flip-Flop


- The output state of a master-slave SR flip-flop is undefined upon returning the control input to 0 when $S = R = 1$.
 - Necessary to avoid this condition.
- Master-slave JK flip-flop allows its two information input lines to be simultaneously 1.
 - Results in toggling the output of the flip flop.

Master-Slave JK Flip-Flop

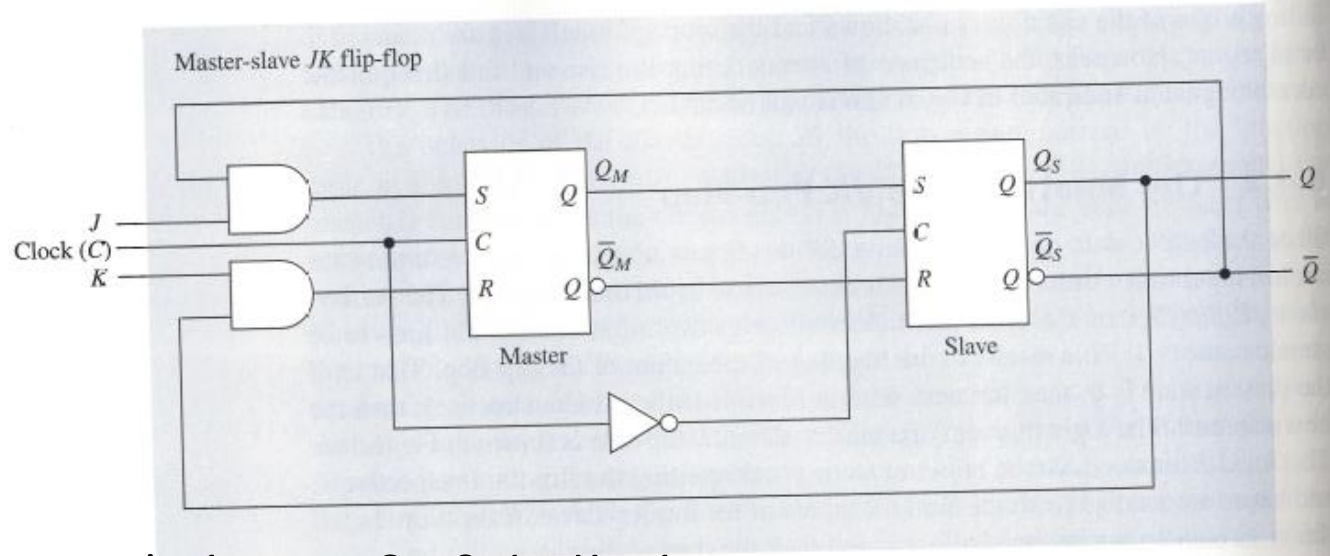

- Assume in 1-state, $C = 0, J = K = 1$.
 - Due to feedback, the output of the J-gate is 0, output of K-gate is 1.
 - If clock is changed to $C = 1$ then master is reset.
- Assume in 0-state, $C = 0, J = K = 1$.
 - Due to feedback, the output of the J-gate is 1, output of K-gate is 0.
 - If clock is changed to $C = 1$ then master is set.
- 1 on J input line, 0 on K input line sets the flip-flop.
 - If in 1-state, unchanged b/c S,R set to 0.
 - If in 0-state, S set to 1, R set to 0.
- 0 on J input, 1 on K input line resets the flip-flop. Why?



Master-Slave JK Flip-Flop

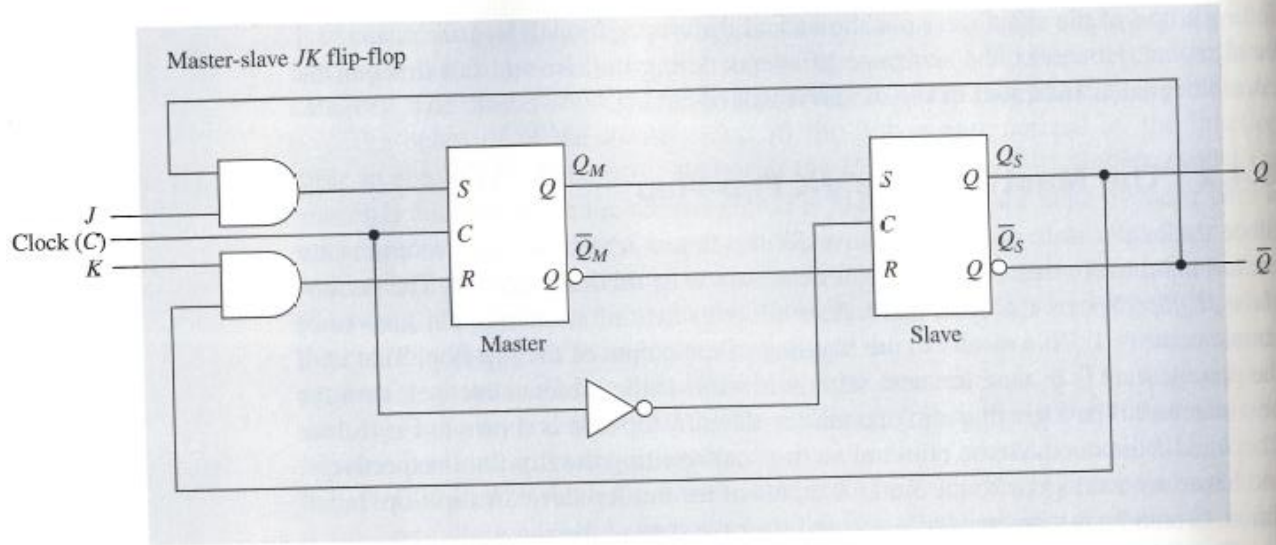

(a)


Inputs			Outputs	
J	K	C	Q^+	\bar{Q}^+
0	0		Q	\bar{Q}
0	1		0	1
1	0		1	0
1	1		\bar{Q}	Q
X	X	0	Q	\bar{Q}

(b)

  

(c)

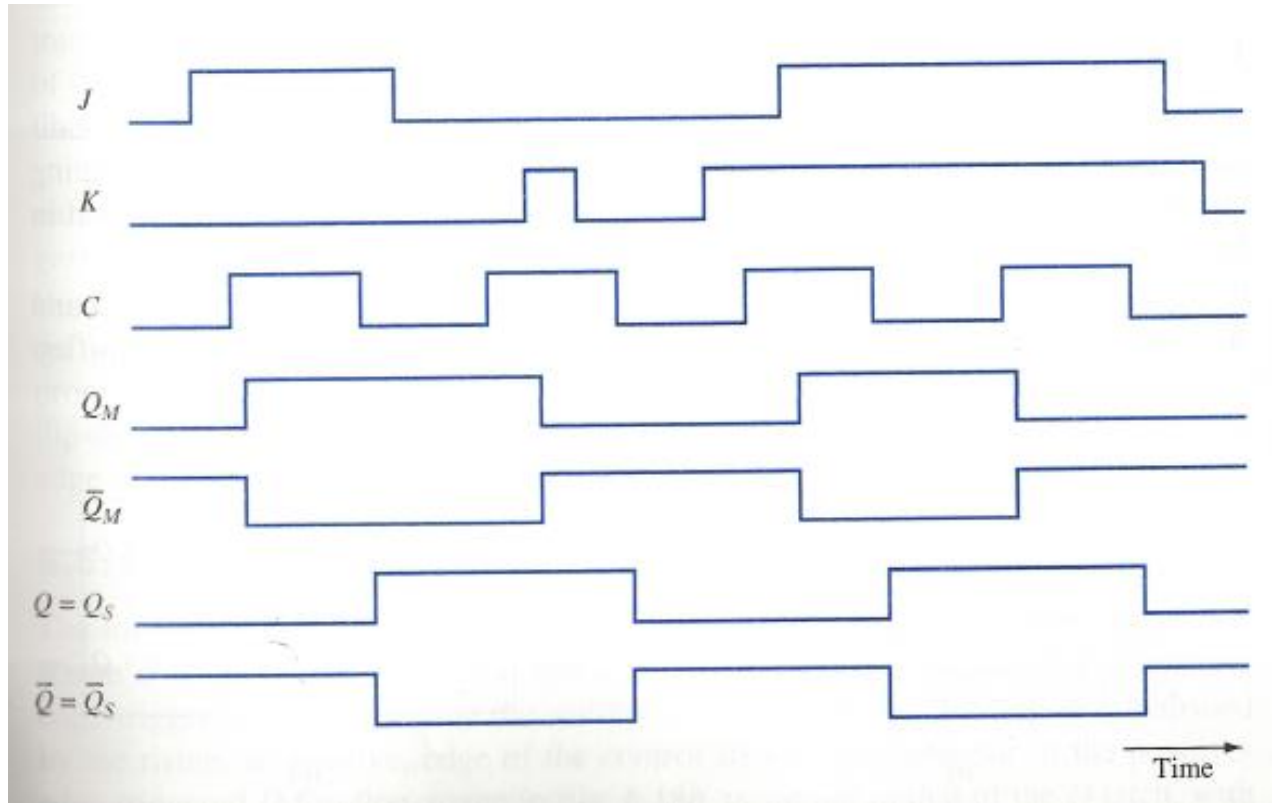
Timing Diagram for Master-Slave JK Flip-Flop



0's and 1's Catching

- The master is enabled during the entire period the control-signal is 1.
- If the slave latch is in its 1-state, then a logic-1 on K-input line causes the master-latch to reset. Slave becomes reset when control signal returns to 0.
- This is known as 0's catching (2nd pulse).
 - Note: if a subsequent 1-signal on J input line and C is still 1, master does not become set again (due to feedback not changing).
- If slave latch is in 0-state, logic-1 on J input line while control signal is 1 causes the master latch to be set and slave will be set upon occurrence of the falling edge.
- This is known as 1's catching (3rd pulse).
- In many applications, 0's and 1's catching behavior is undesirable. Normally recommended that the J and K input values should be held fixed during the entire interval the master is enabled.
- Any changes in J, K must occur while the control signal is 0.

0's Catching

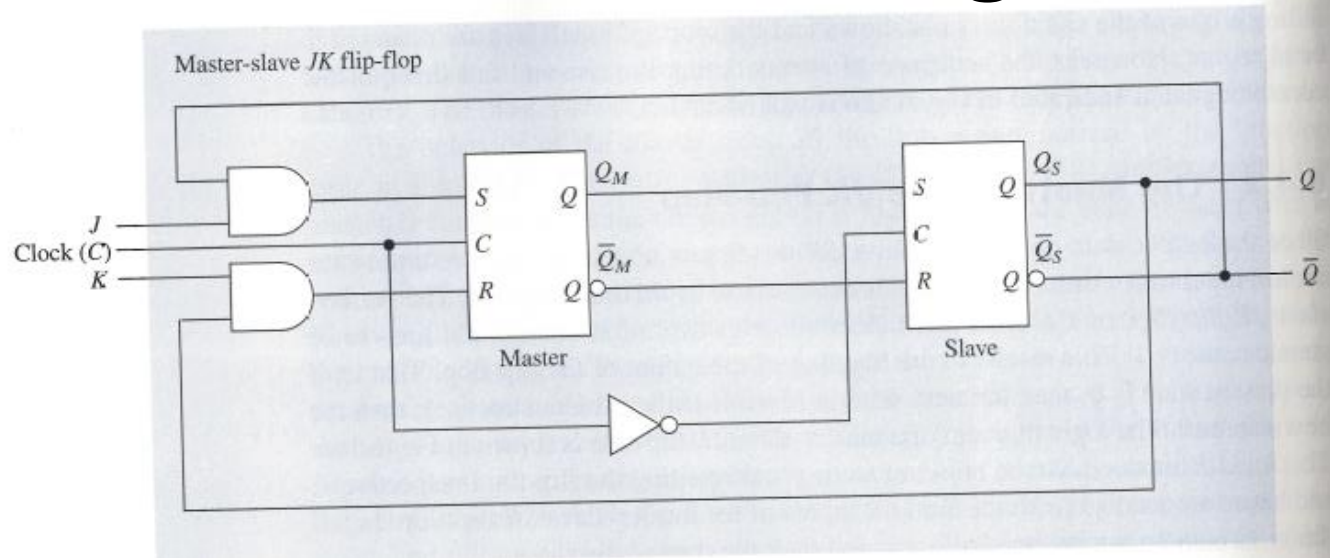

- Assume in 1-state ($Q = 1, \bar{Q} = 0$), $C = 1, J = 0, K = 0$
- K gets set to 1 briefly.
 - Master gets reset, Slave will become reset when Clock goes to 0.
- K goes to 0.
- J goes to 1. What happens?
- Nothing! Slave will still become reset when Clock goes to 0.
- Why?