

# Digital Logic Design

## ENEE 244-010x

### Lecture 22

# Announcements

- Make sure you are up-to-date with material covered last time (on 11/25).
- Homework 9 up on course webpage, due on Monday, 12/7
  - Final homework assignment
- Please fill out Course Evaluations online.
  - Class time on Monday, 12/7
  - Make sure to bring in laptop, phone, etc.

# Agenda


- Last Time:
  - Modeling Clocked Synchronous Sequential Network Behavior (7.3)
  - Started State Table Reduction (7.4)
- This time:
  - Quick review of state diagrams (7.3)
  - State Table Reduction (7.4)
  - The State Assignment (7.5)
  - Completing the Design of Clocked Synchronous Sequential Networks (7.6)

# Modeling clocked synchronous sequential network behavior


- Approach for the synthesis of clocked synchronous sequential networks:
  - State table/state diagram is constructed from word specifications.
  - State reduction technique to obtain a state table with minimum number of states.
  - Transition table is formed by coding the states of the state table.
  - Excitation table is constructed based on the flip-flop types to be used.
  - From the excitation table, the excitation and output expressions for the network are determined.
  - Finally, the logic diagram is drawn.

# Examples of Modeling Step
 
# State Diagram for Mealy serial binary adder



(a)

 


(b)

**Figure 7.12** Obtaining the state diagram for a Mealy serial binary adder.  
(a) Partial state diagram.  
(b) Completed state diagram.

# State Diagram for a Sequence Recognizer

- Network produces a 1 output iff the current input and the previous three inputs correspond to 010.
- 010 Sequence Recognizer
- The 1 output is to occur at the time of the third input of the recognized sequence. Outputs of 0 are to be produced at all other times.
- A Mealy network model is developed since the output is a function of the current input  $x$ .
- Network is not required to reset upon the occurrence of the fourth input.
- Sequences may overlap.
 
# State Diagram for a Sequence Recognizer (010)



Can we reduce the number of states?  
How do we know?




# Determining Equivalent Pairs of States

Theorem:


Two states  $p$  and  $q$  of a clocked synchronous sequential network are equivalent iff for each combination of values of the input variables

1. Their outputs are identical
2. Their next states are equivalent

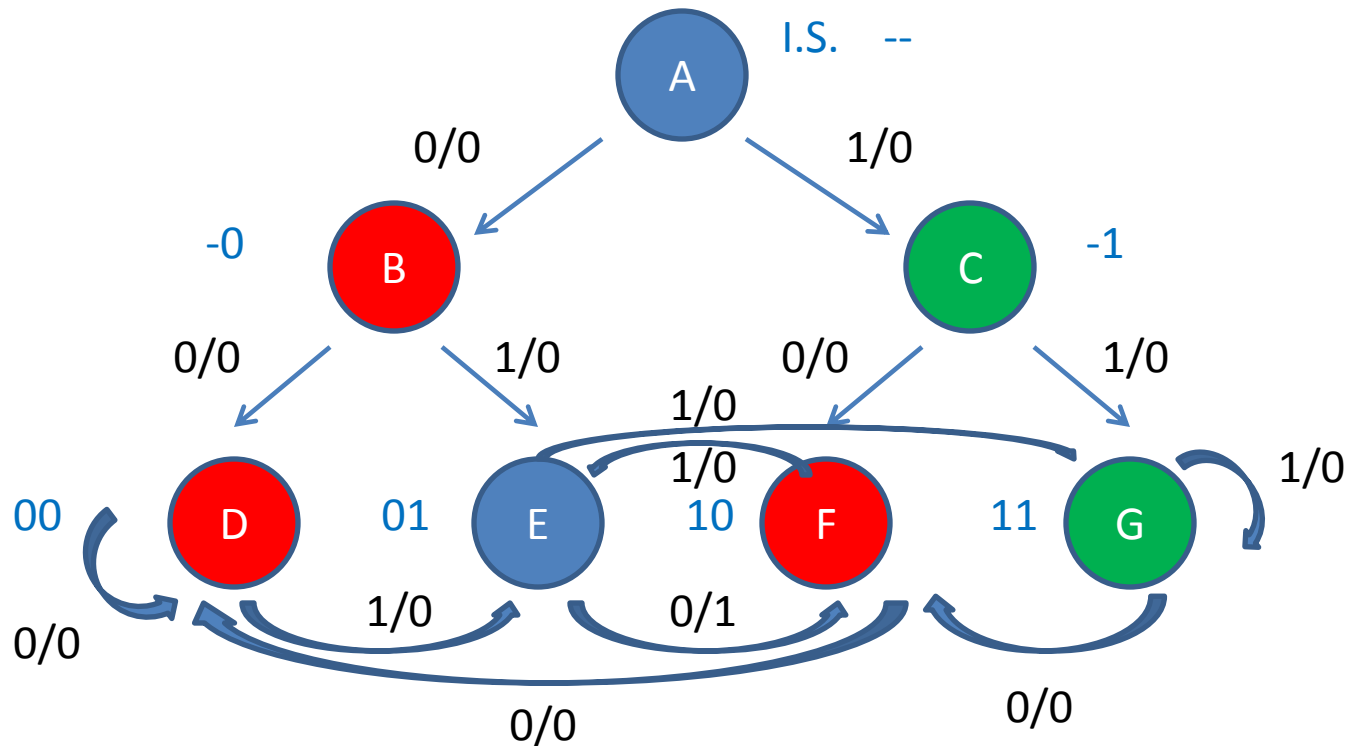
# State Diagram for a Sequence Recognizer (010)


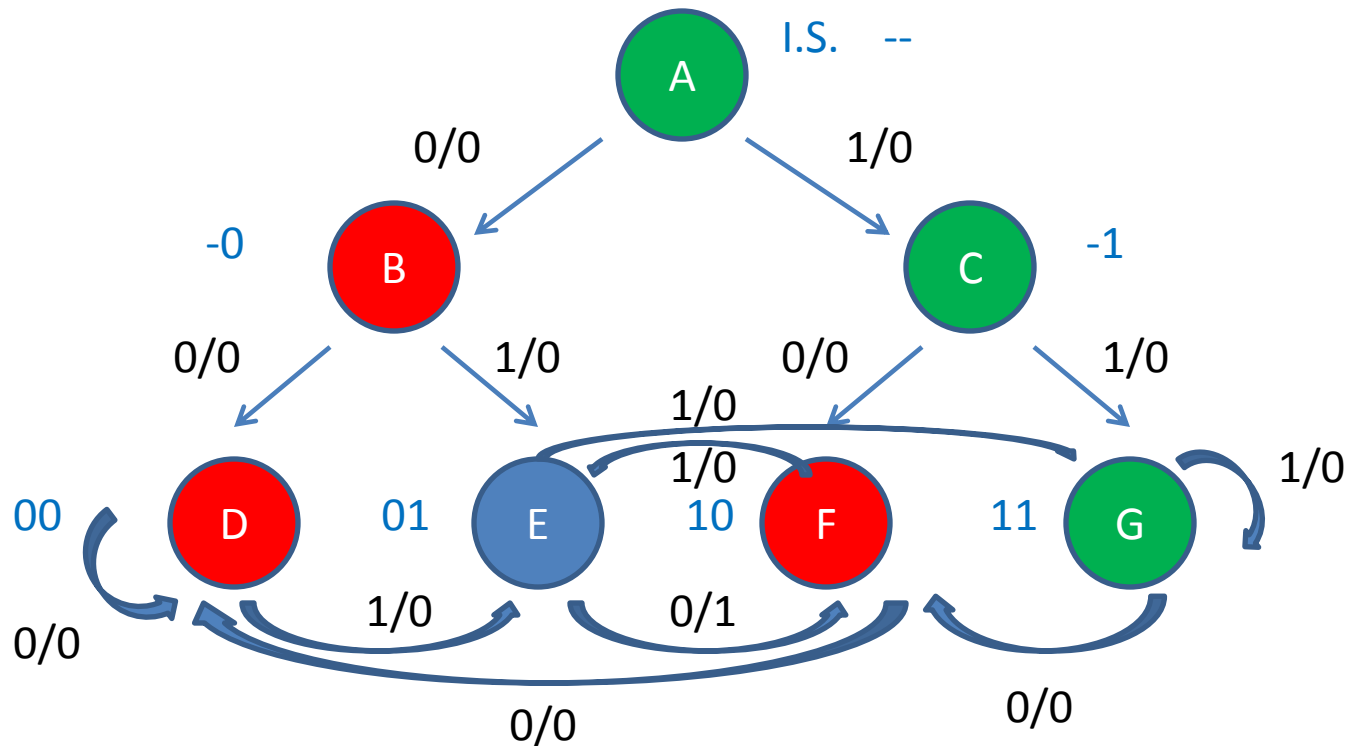
# State Diagram for a Sequence Recognizer (010)



 
# State Diagram for a Sequence Recognizer (010)



# Algorithm for Determining Equivalent Pairs of States

- Uses an **implication table**

 

**Figure 7.19** The structure of an implication table.

$q_1, \dots, q_n$  are the states of the state table. There is one cell in the implication table for each pair of distinct cells.




# Algorithm for Determining Equivalent Pairs of States

1. Place a  $\times$  in the  $(q_i, q_j)$ -cell if the outputs are contradictory for some input. If there are no contradictory outputs then enter the pair of next states for each input. If neither a  $\times$  nor pairs of states are entered in the cell, then a check mark is inserted (denoting equivalence of the two states).
2. All state pair entries are inspected by the following process:
  - If  $(q_a, q_b)$  is an entry in the  $(q_i, q_j)$ -cell and if the  $(q_a, q_b)$ -cell contains an  $\times$  then an  $\times$  is placed in the the  $(q_i, q_j)$ -cell and all other entries are ignored.
  - Otherwise, process is repeated on one of these other state pairs.
  - \*\*Next-state pairs of the form  $(q_i, q_j)$ ,  $(q_j, q_i)$  or  $(q_k, q_k)$  are not entered.
3. Repeat Step 2 until it is possible to make an entire pass of the implication table without any additional  $\times$  being entered. If the  $(q_i, q_j)$ -cell has no  $\times$  at this time, then  $q_i \equiv q_j$ .

# Example of Algorithm

**Table 7.13** Example of a state table in which state reduction can be performed

Present state	Next state		Output (z)	
	Input (x)		Input (x)	
	0	1	0	1
*A	A	B	0	0
B	D	C	0	1
C	F	E	0	0
D	D	F	0	0
E	B	G	0	0
F	G	C	0	1
G	A	F	0	0

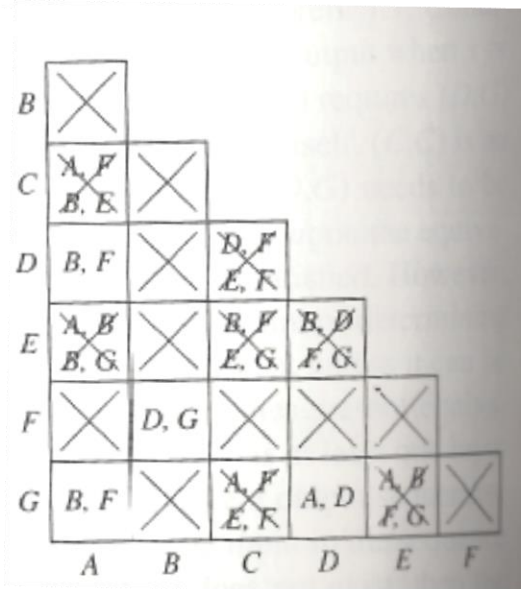  

# Example for Implication Table

B	X					
C	<del>A, F</del> <del>B, E</del>	X				
D	B, F	X	<del>D, F</del> <del>E, F</del>			
E	<del>A, B</del> <del>B, G</del>	X	<del>B, F</del> <del>E, G</del>	<del>B, D</del> <del>F, G</del>		
F	X	D, G	X	X	X	
G	B, F	X	<del>A, F</del> <del>E, F</del>	A, D	<del>A, B</del> <del>F, G</del>	X
	A	B	C	D	E	F

1. (D, G)
2. (D, G), (B, F)
3. (A, D, G), (B, F)
4. (A, D, G), (B, F), (C), (E)



# Constructing the Minimal State Table

**Table 7.13** Example of a state table in which state reduction can be performed

Present state	Next state		Output (z)	
	Input (x)		Input (x)	
	0	1	0	1
*A	A	B	0	0
B	D	C	0	1
C	F	E	0	0
D	D	F	0	0
E	B	G	0	0
F	G	C	0	1
G	A	F	0	0

**Table 7.14** Minimal state table for Table 7.13

Present state		Next state		Output (z)	
		Input (x)		Input (x)	
		0	1	0	1
(A,D,G):	* $\alpha$	$\alpha$	$\beta$	0	0
(B,F):	$\beta$	$\alpha$	$\gamma$	0	1
(C):	$\gamma$	$\beta$	$\delta$	0	0
(E):	$\delta$	$\beta$	$\alpha$	0	0