

Class Exercise—Building a 3-bit Lookahead Adder

10/26/15

Recall: The i -th binary adder has inputs x_i, y_i, c_i


For $i > 1$, instead of waiting for c_i to propagate, we would like to compute it ahead of time.

We have the following formulas:

$$\begin{aligned} g_i &= x_i y_i \\ p_i &= x_i + y_i \\ c_{i+1} &= g_i + p_i c_i \end{aligned}$$

Finally, $s_i = c_i \oplus x_i \oplus y_i$

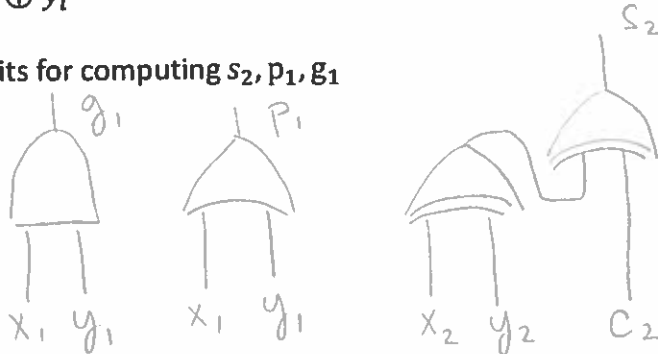1. Draw the circuits for computing s_2, p_1, g_1



2. Draw the circuit for computing c_2 given input wires corresponding to p_0, g_0, p_1, g_1, c_0 .

$$\begin{aligned} c_2 &= g_1 + p_1 c_1 \\ &= g_1 + p_1 (g_0 + p_0 c_0) \\ &= g_1 + p_1 g_0 + p_1 p_0 c_0 \end{aligned}$$



3. Draw the circuit diagram for the 3-bit lookahead adder by combining 1 and 2 and the 2-bit lookahead adder (you can add on to your diagram from the previous page).

4. How many time steps does it take to compute the final 4-bit sum?

$$4 \left\{ \begin{array}{l} 1 \text{ time unit to compute } p_0, g_0, p_1, g_1 \\ 2 \text{ time units to compute } c_1, c_2, c_3 \\ 1 \text{ time unit to propagate } c_1, c_2 \text{ to final outputs } s_2, s_1 \end{array} \right.$$

Solutions

Class Exercise—Building a 2-bit Lookahead Adder

10/26/15

Recall: The i -th binary adder has inputs x_i, y_i, c_i

For $i > 1$, instead of waiting for c_i to propagate, we would like to compute it ahead of time.

We have the following formulas:


$$g_i = x_i y_i$$

$$p_i = x_i \oplus y_i$$

$$c_{i+1} = g_i + p_i c_i$$

Finally, $s_i = c_i \oplus x_i \oplus y_i$

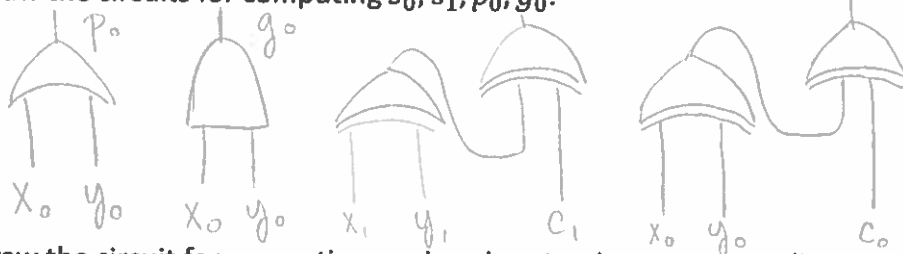1. Draw the circuits for computing s_0, s_1, p_0, g_0 .



2. Draw the circuit for computing c_1 given inputs wires corresponding to p_0, g_0, c_0 .



3. Draw the circuit diagram for the 2-bit lookahead adder by combining 1 and 2.

