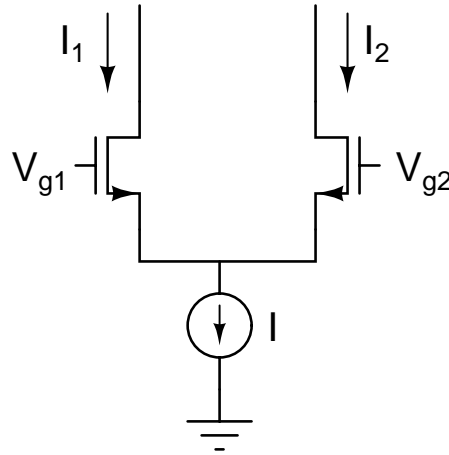


<http://www.ece.umd.edu/~pabshire/enee312h.htm>

due Wednesday, May 8, 2002

- 1) Consider the MOS differential pair with inputs  $V_{g1}$  and  $V_{g2}$ , biased with a current  $I$  so that both transistors operate in weak inversion, as shown in the following figure:



- Derive a transfer characteristic that expresses the difference in drain currents  $\Delta I = I_1 - I_2$  as a function of the differential input voltage  $\Delta V = V_{g1} - V_{g2}$  and the bias current  $I$ . You may neglect the Early effect and the body effect for this calculation.
  - What common scientific function does this two transistor circuit implement?
  - For a sufficiently small input signal, there is a linear relationship between the input  $\Delta V$  and output  $\Delta I$ . Over what range of input signals  $\Delta V$  is this linear relationship valid? What is the transconductance  $\partial \Delta I / \partial \Delta V$  at the midpoint of this range?
- 2) – 8) Complete Sedra & Smith problems 5.49, 5.65, 5.81, 5.114, 6.85, 6.87, 6.88

**Research Question:**

One method for performing a multiplication of two analog input values is to use a translinear circuit, as explored in previous homeworks. Another widely known and important method is the six-transistor Gilbert multiplier circuit, first described in the paper by Barrie Gilbert, "A Precise Four-Quadrant Multiplier with Subnanosecond Response," IEEE Journal of Solid State Circuits, Vol. SC-3, pp. 365-373, Dec 1968. Adapt the Gilbert multiplier circuit to use MOS transistors rather than BJTs, and use your results from Problem 1) above to determine the differential output current  $\Delta I$  as a function of the differential input voltages  $\Delta V_1$  and  $\Delta V_2$ .